

EN2042102 วงจรไฟฟ้าและอิเล็กทรอนิกส์

Circuits and Electronics



บทที่ 4 ทฤษฎีโครงข่ายไฟฟ้า

Electrical Network Theorems



สาขาวิชาวิศวกรรมคอมพิวเตอร์

คณะวิศวกรรมศาสตร์ มหาวิทยาลัยเทคโนโลยีราชมงคลพระนคร



# OBJECTIVES



- ❖ Become familiar with the superposition theorem and its unique ability to separate the impact of each source on the quantity of interest.
- ❖ Be able to apply Thévenin's theorem to reduce any two-terminal, series-parallel network with any number of sources to a single voltage source and series resistor.
- ❖ Become familiar with Norton's theorem and how it can be used to reduce any two-terminal, seriesparallel network with any number of sources to a single current source and a parallel resistor.



# OBJECTIVES

- ❖ Understand how to apply the maximum power transfer theorem to determine the maximum power to a load and to choose a load that will receive maximum power.
- ❖ Become aware of the reduction powers of Millman's theorem and the powerful implications of the substitution and reciprocity theorems.





# SUPERPOSITION THEOREM



- ❖ The **superposition theorem** is unquestionably one of the most powerful in this field.
- ❖ It has such widespread application that people often apply it without recognizing that their maneuvers are valid only because of this theorem.



# SUPERPOSITION THEOREM



❖ In general, the theorem can be used to do the following:

- *Analyze networks such as introduced in the last chapter that have two or more sources that are not in series or parallel.*
- *Reveal the effect of each source on a particular quantity of interest.*
- *For sources of different types (such as dc and ac, which affect the parameters of the network in a different manner) and apply a separate analysis for each type, with the total result simply the algebraic sum of the results.*



# SUPERPOSITION THEOREM




❖ The superposition theorem states the following:

- *The current through, or voltage across, any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source.*




# SUPERPOSITION THEOREM

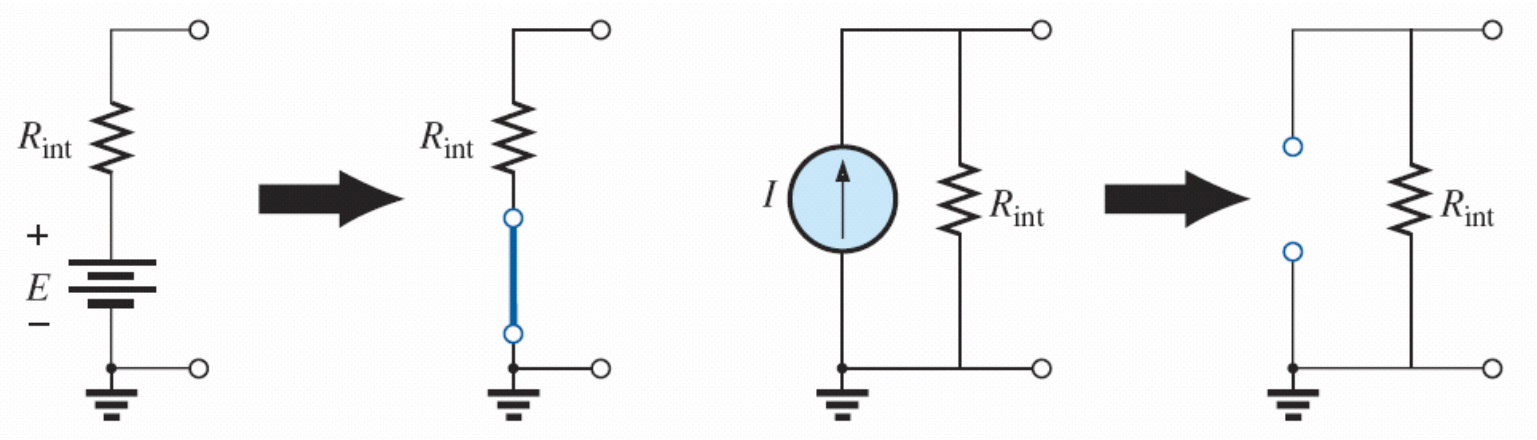


**FIG. 9.1** Removing a voltage source and a current source to permit the application of the superposition theorem.



# SUPERPOSITION THEOREM

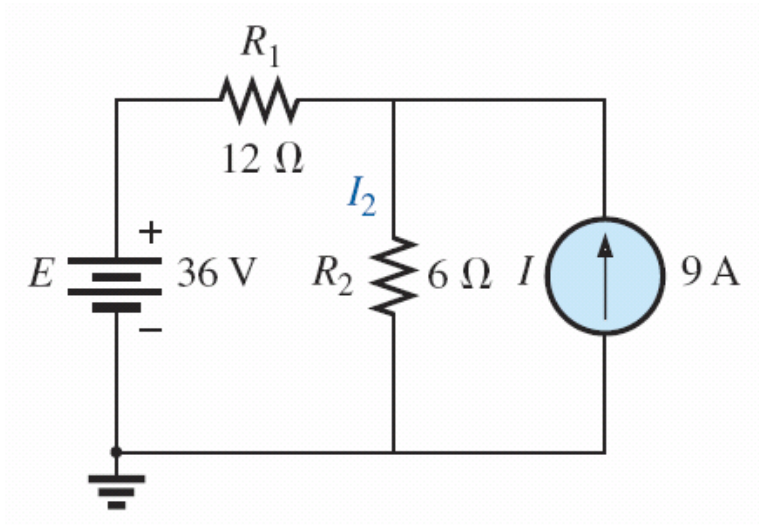

**FIG. 9.2** Network to be analyzed in Example 9.1 using the superposition theorem.

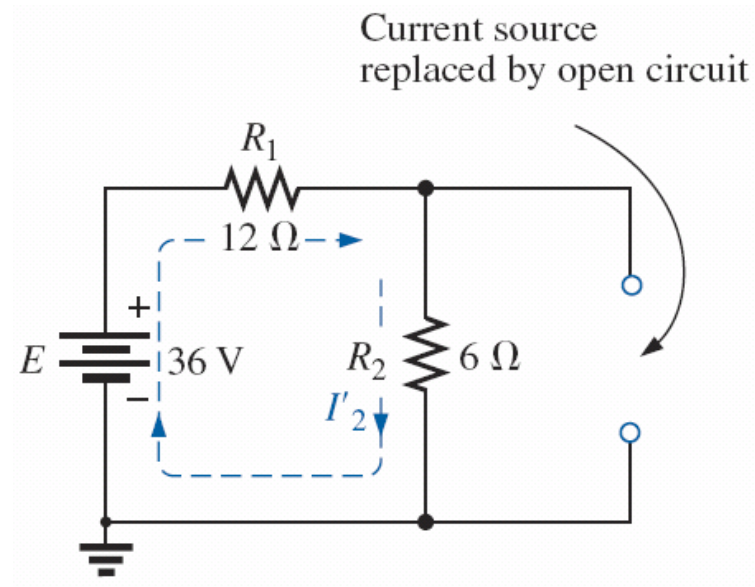

**FIG. 9.3** Replacing the 9 A current source in Fig. 9.2 by an open circuit to determine the effect of the 36 V voltage source on current  $I_2$ .





# SUPERPOSITION THEOREM

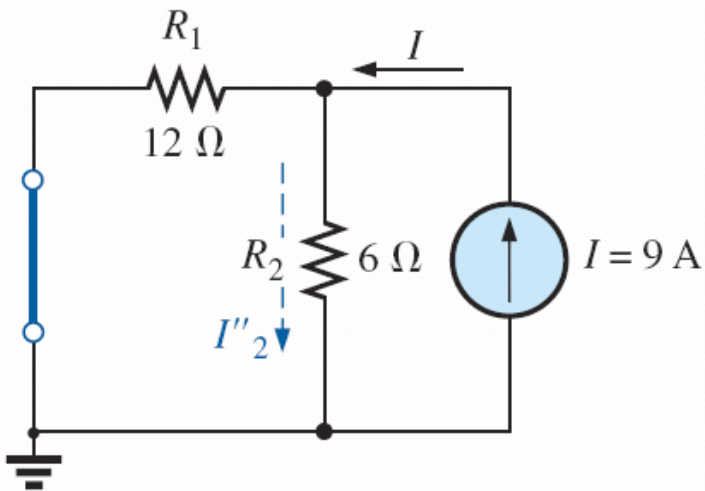


FIG. 9.4 Replacing the 36 V voltage source by a short-circuit equivalent to determine the effect of the 9 A current source on current  $I_2$ .


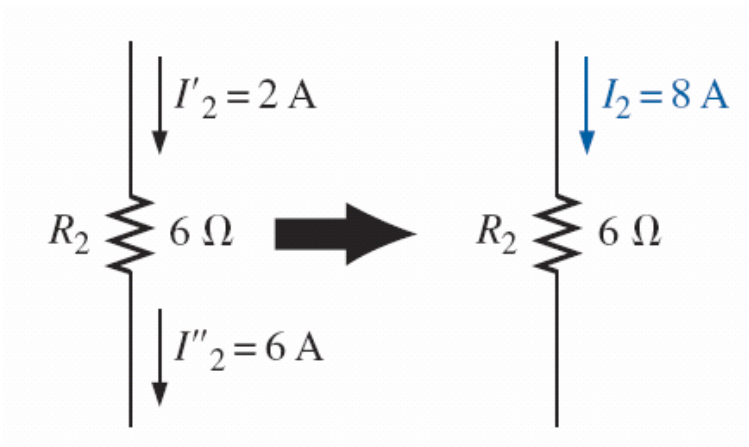


FIG. 9.5 Using the results of Figs. 9.3 and 9.4 to determine current  $I_2$  for the network in Fig. 9.2.

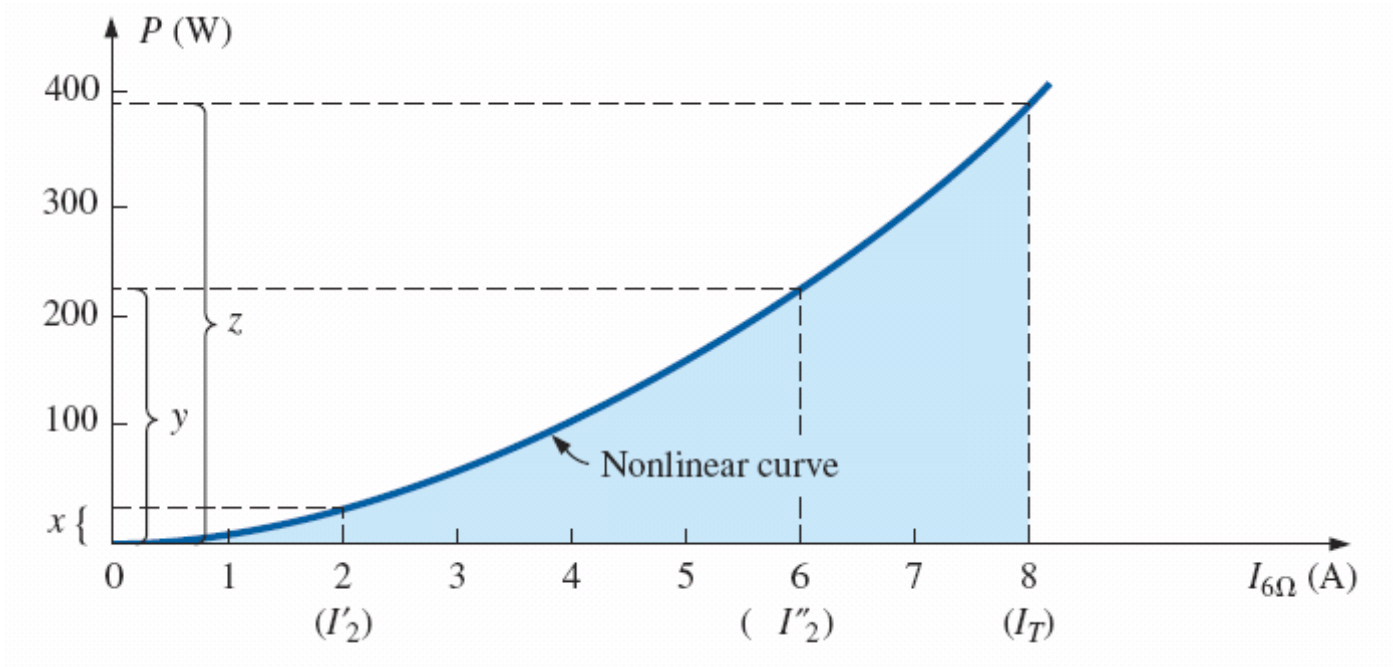

# SUPERPOSITION THEOREM



**FIG. 9.6** Plotting power delivered to the  $6\Omega$  resistor versus current through the resistor.



# SUPERPOSITION THEOREM


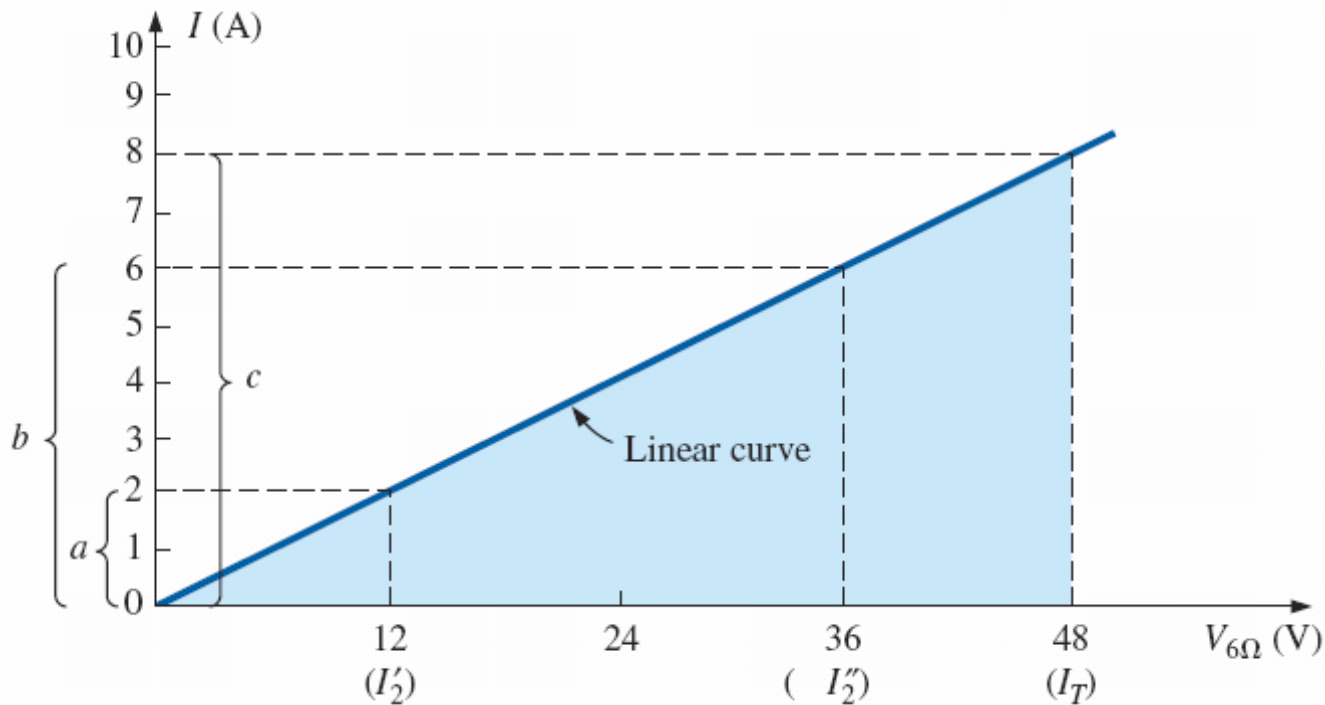


FIG. 9.7 Plotting  $I$  versus  $V$  for the  $6\Omega$  resistor.

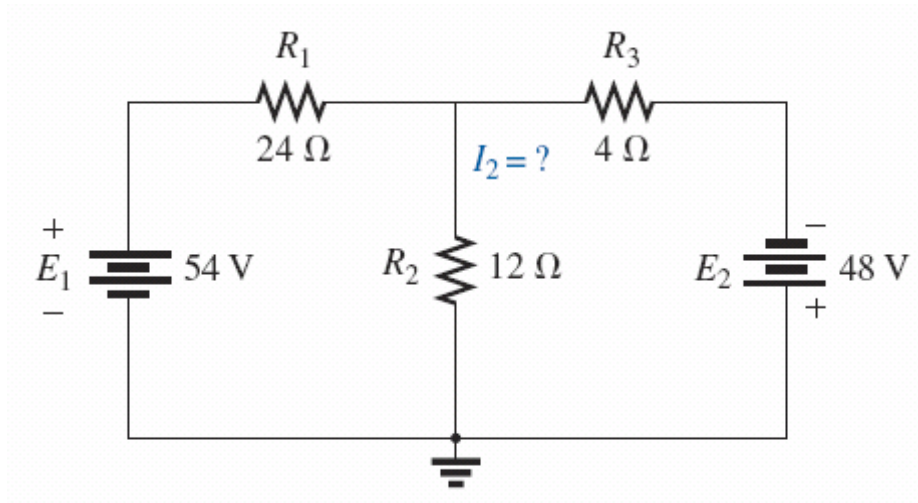


# SUPERPOSITION THEOREM



**FIG. 9.8** Using the superposition theorem to determine the current through the 12 $\Omega$  resistor (Example 9.2).




# SUPERPOSITION THEOREM

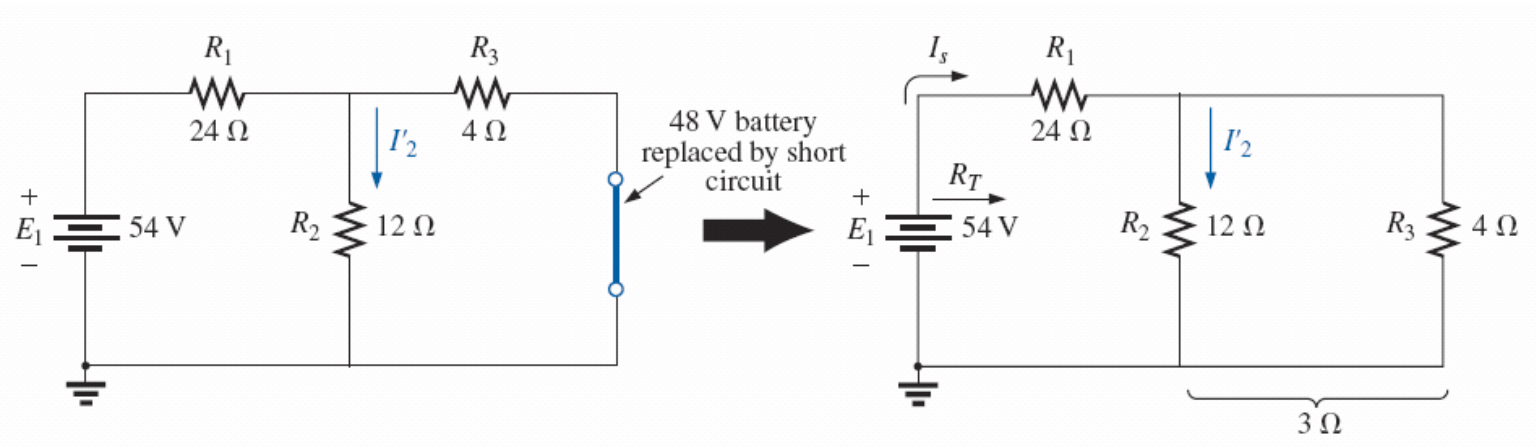

**FIG. 9.9** Using the superposition theorem to determine the effect of the 54 V voltage source on current  $I_2$  in Fig. 9.8.




# SUPERPOSITION THEOREM

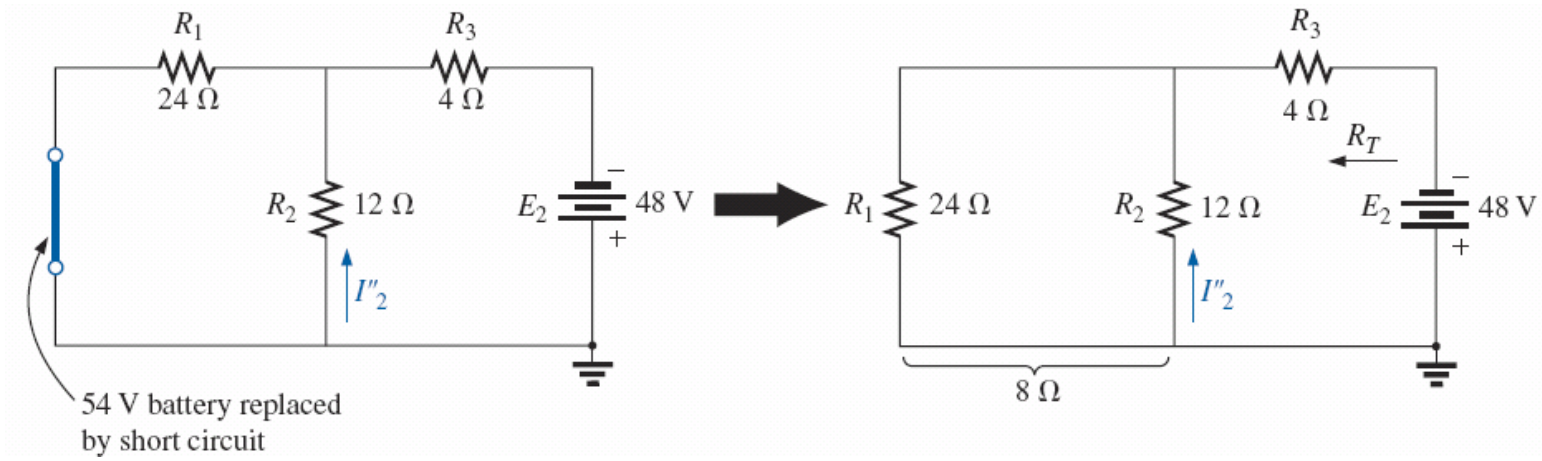

**FIG. 9.10** Using the superposition theorem to determine the effect of the 48 V voltage source on current  $I_2$  in Fig. 9.8.




# SUPERPOSITION THEOREM

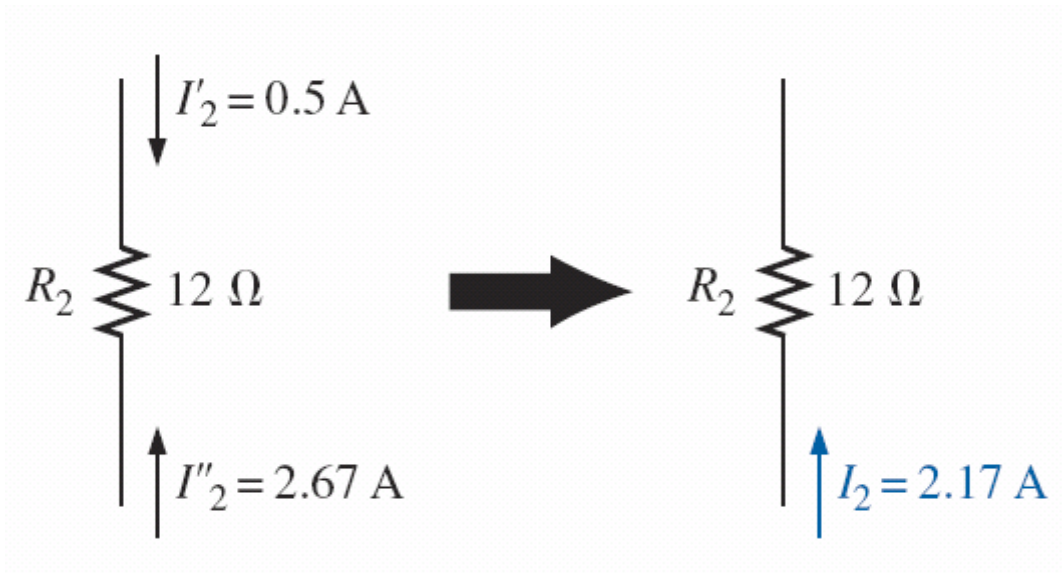


**FIG. 9.11** Using the results of Figs. 9.9 and 9.10 to determine current  $I_2$  for the network in Fig. 9.8.



# SUPERPOSITION THEOREM

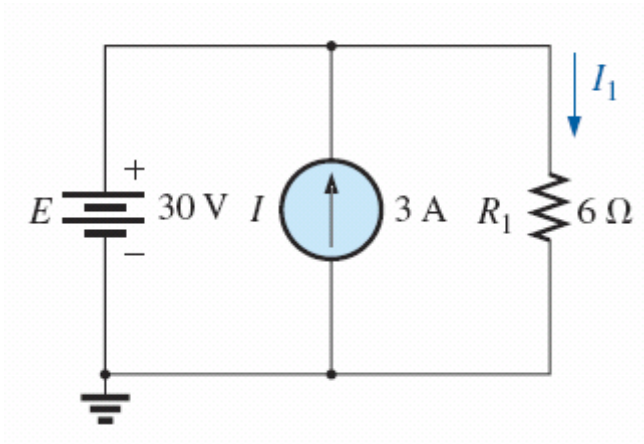

**FIG. 9.12** Two-source network to be analyzed using the superposition theorem in Example 9.3.

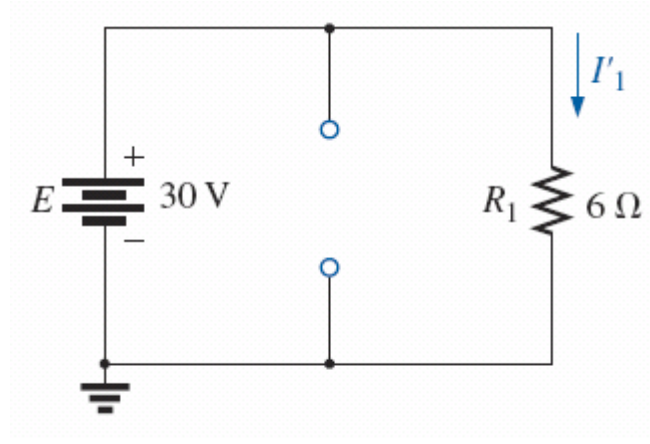


**FIG. 9.13** Determining the effect of the 30 V supply on the current  $I_1$  in Fig. 9.12.






# SUPERPOSITION THEOREM

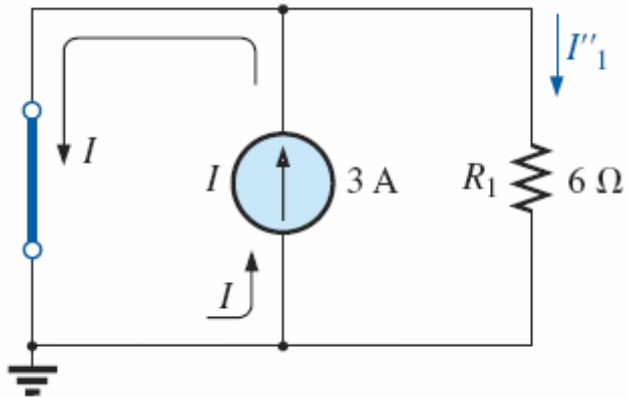

**FIG. 9.14** Determining the effect of the 3 A current source on the current  $I_1$  in Fig. 9.12.

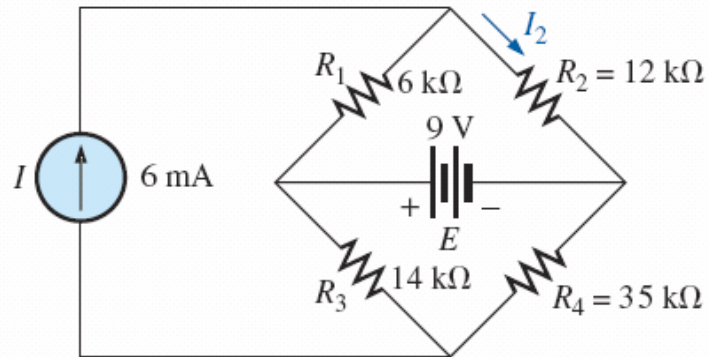

**FIG. 9.15** Example 9.4.



# SUPERPOSITION THEOREM

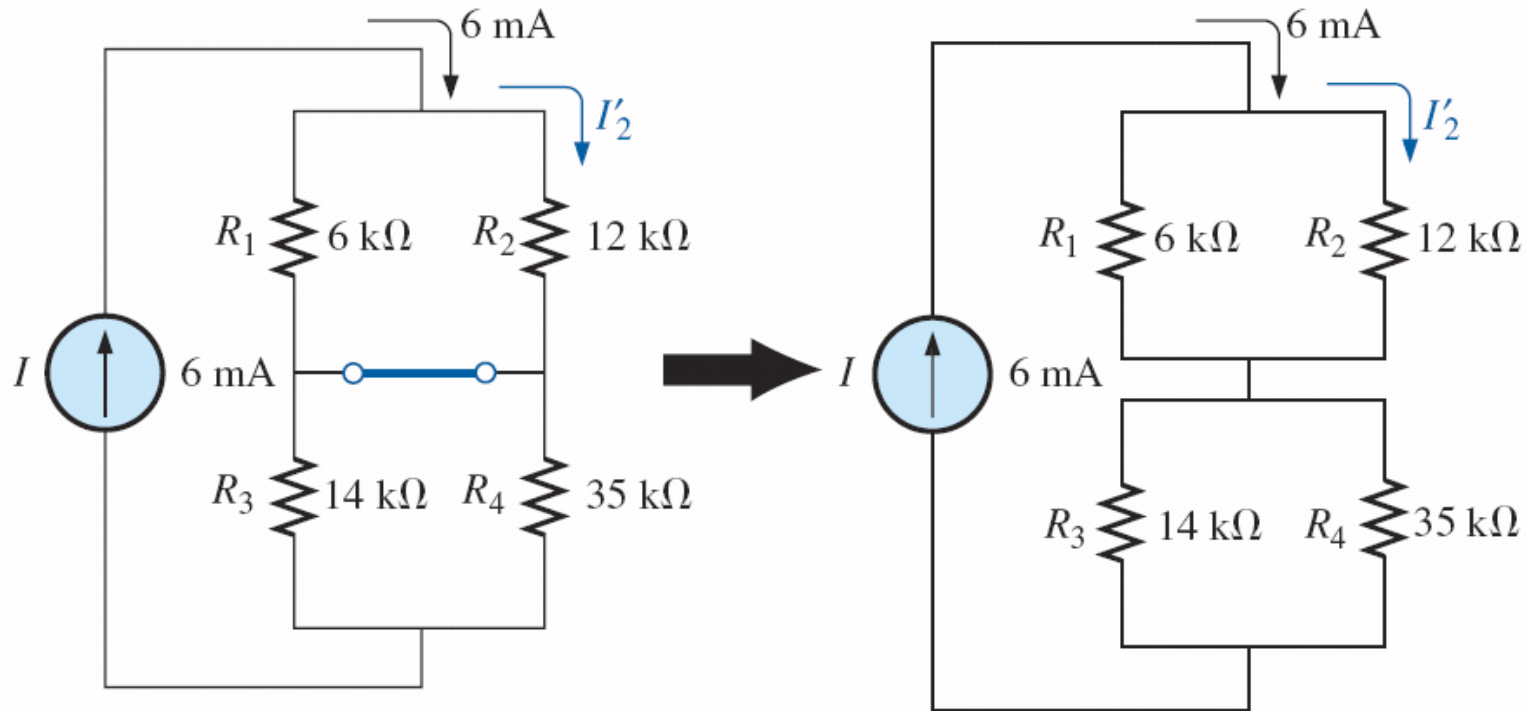


FIG. 9.16 The effect of the current source  $I$  on the current  $I_2$ .



# SUPERPOSITION THEOREM

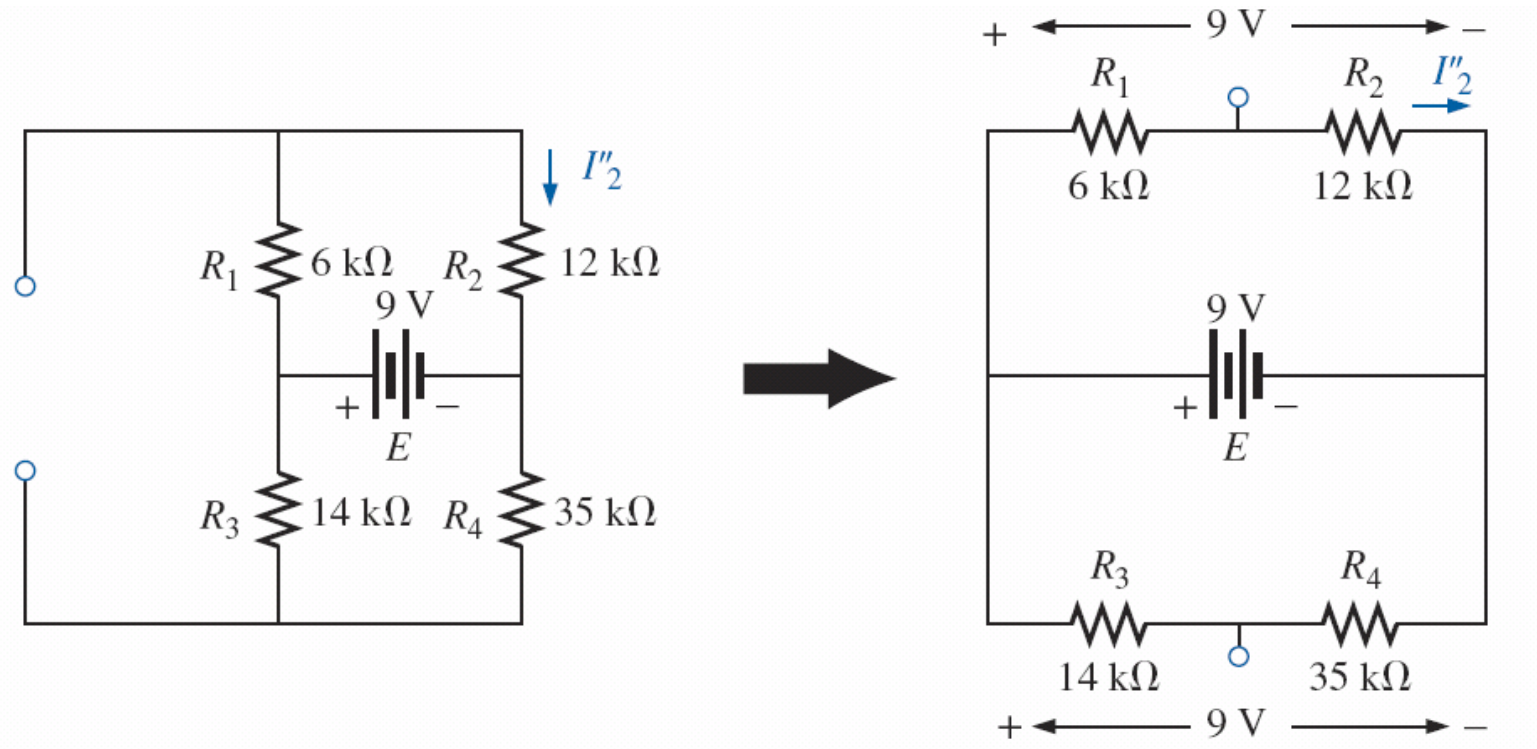


FIG. 9.17 The effect of the voltage source  $E$  on the current  $I_2$ .



# SUPERPOSITION THEOREM

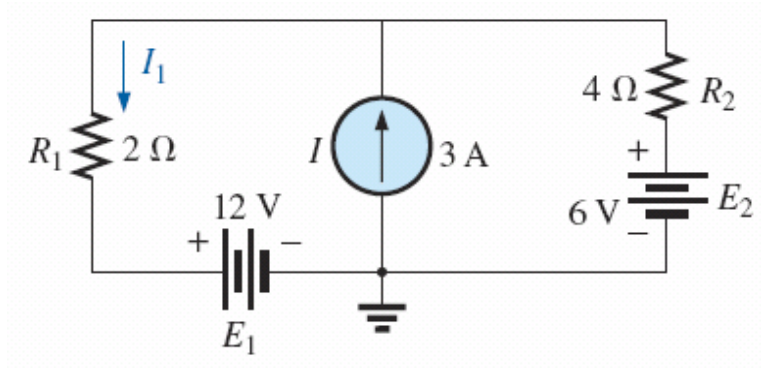


FIG. 9.18 Example 9.5.

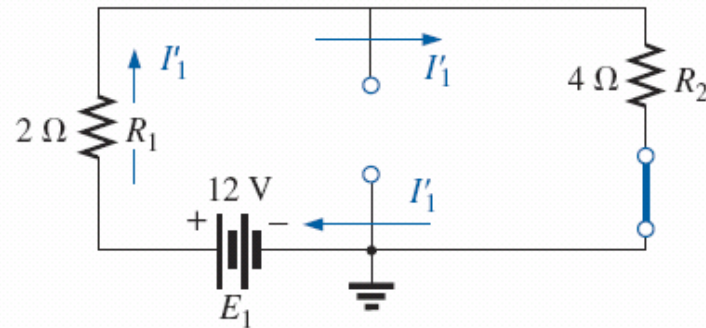


FIG. 9.19 The effect of  $E_1$  on the current  $I$ .



# SUPERPOSITION THEOREM

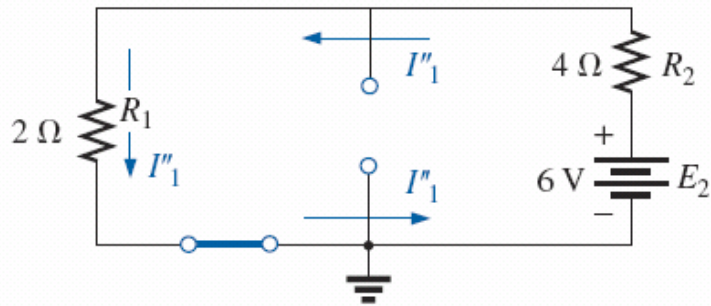


FIG. 9.20 The effect of  $E_2$  on the current  $I_1$ .

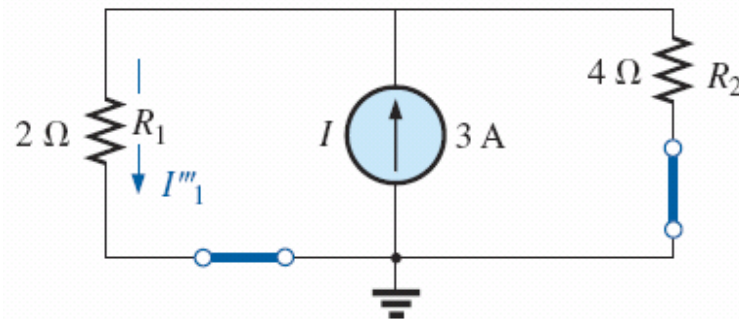


FIG. 9.21 The effect of  $I$  on the current  $I_1$ .



# SUPERPOSITION THEOREM

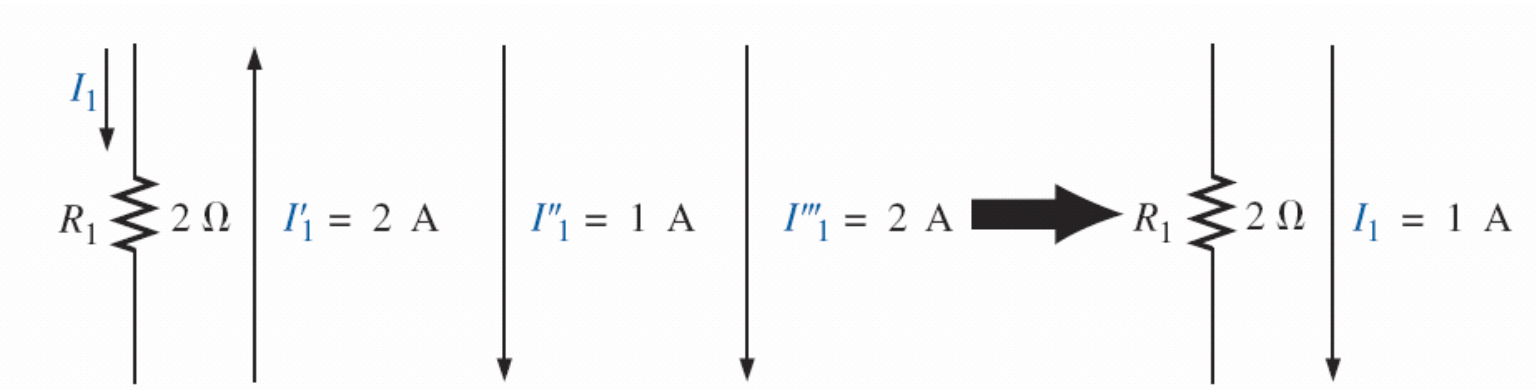


FIG. 9.22 The resultant current  $I_1$ .



# THÉVENIN'S THEOREM

- ❖ The next theorem to be introduced, **Thévenin's theorem**, is probably one of the most interesting in that it permits the reduction of complex networks to a simpler form for analysis and design.





# THÉVENIN'S THEOREM

❖ In general, the theorem can be used to do the following:

- *Analyze networks with sources that are not in series or parallel.*
- *Reduce the number of components required to establish the same characteristics at the output terminals.*
- *Investigate the effect of changing a particular component on the behavior of a network without having to analyze the entire network after each change.*







# THÉVENIN'S THEOREM

❖ Thévenin's theorem states the following:

- *Any two-terminal dc network can be replaced by an equivalent circuit consisting solely of a voltage source and a series resistor as shown in Fig. 9.23.*

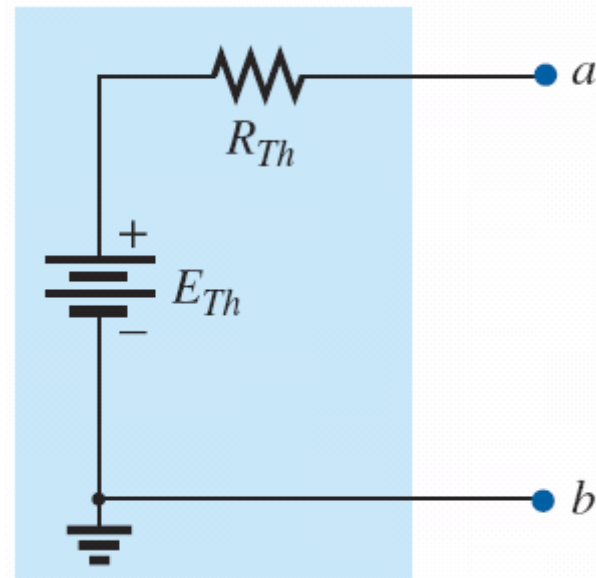


FIG. 9.23 Thévenin equivalent circuit.



# THÉVENIN'S THEOREM

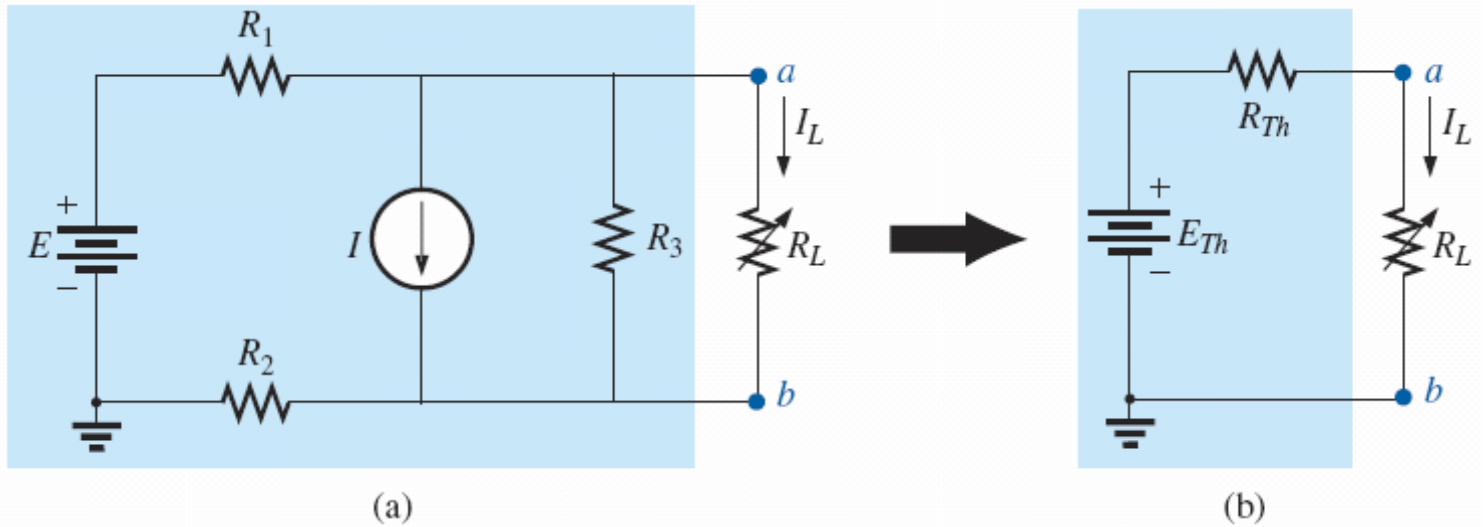


FIG. 9.25 Substituting the Thévenin equivalent circuit for a complex network.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure



### *Preliminary:*

- 1. Remove that portion of the network where the Thévenin equivalent circuit is found. In Fig. 9.25(a), this requires that the load resistor  $R_L$  be temporarily removed from the network.*
- 2. Mark the terminals of the remaining two-terminal network. (The importance of this step will become obvious as we progress through some complex networks.)*





# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure



$R_{Th}$ :

- 3. Calculate  $R_{Th}$  by first setting all sources to zero (voltage sources are replaced by short circuits and current sources by open circuits) and then finding the resultant resistance between the two marked terminals. (If the internal resistance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.)





# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

❖  $E_{Th}$ :



- 4. Calculate  $E_{Th}$  by first returning all sources to their original position and finding the open-circuit voltage between the marked terminals. (This step is invariably the one that causes most confusion and errors. In all cases, keep in mind that it is the open-circuit potential between the two terminals marked in step 2.)



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

### ❖ *Conclusion:*



- *5. Draw the Thévenin equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit. This step is indicated by the placement of the resistor  $R_L$  between the terminals of the Thévenin equivalent circuit as shown in Fig. 9.25(b).*



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

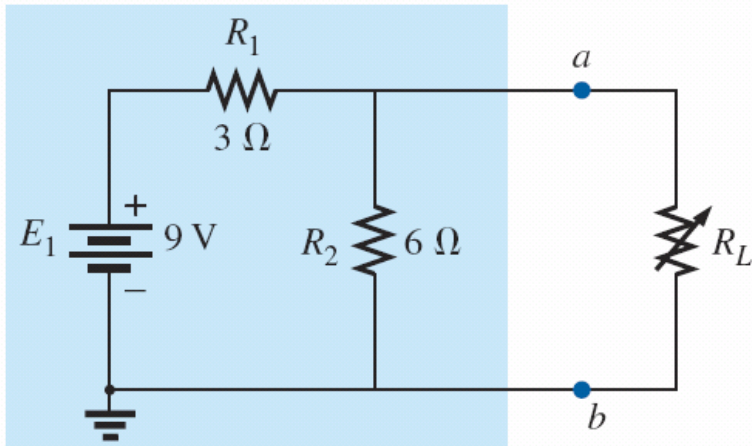


FIG. 9.26 Example 9.6.

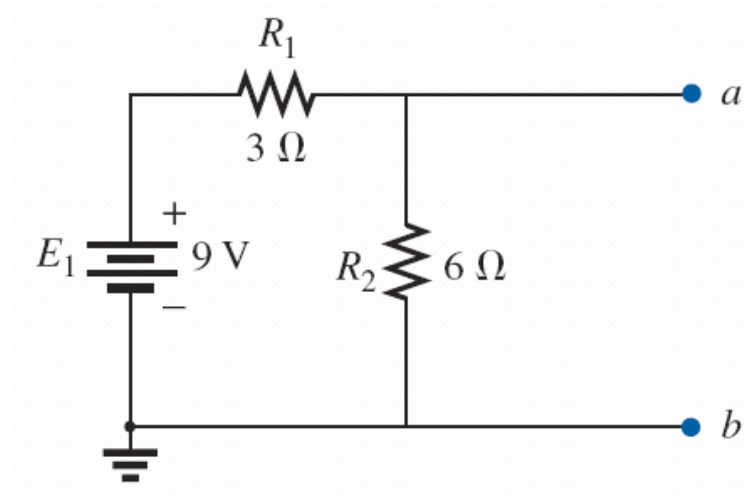


FIG. 9.27 Identifying the terminals of particular importance when applying Thévenin's theorem.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

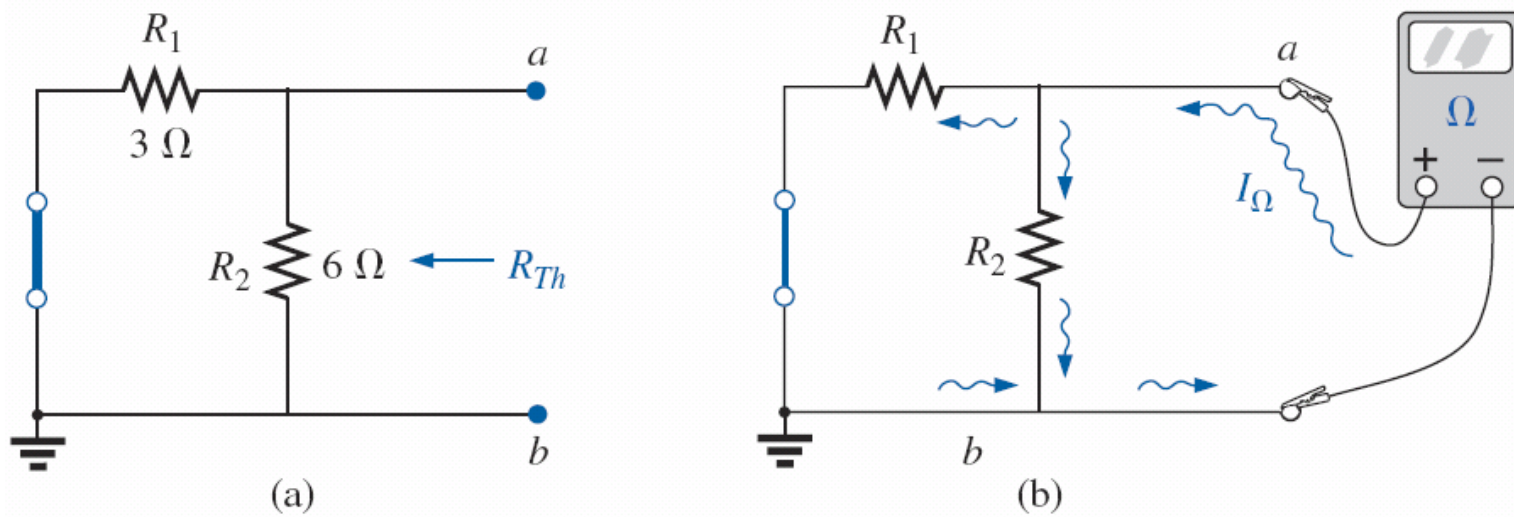


FIG. 9.28 Determining  $R_{Th}$  for the network in Fig. 9.27.





# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

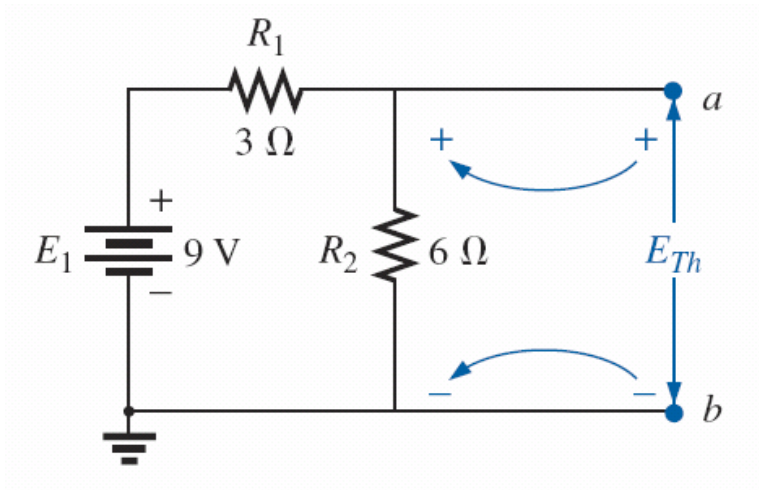


FIG. 9.29 Determining  $E_{Th}$  for the network in Fig. 9.27.

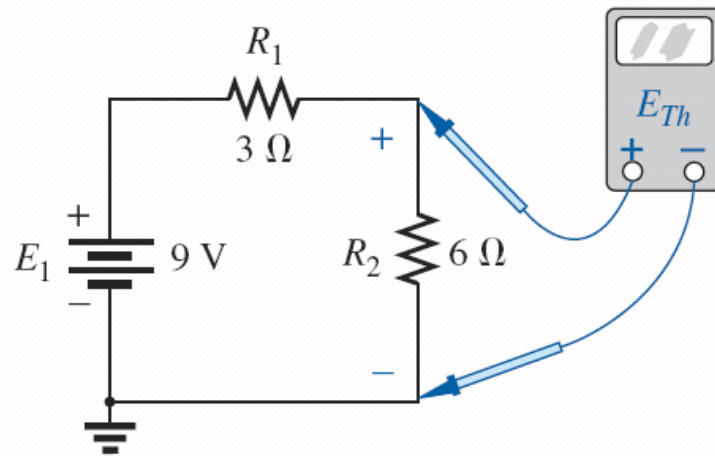


FIG. 9.30 Measuring  $E_{Th}$  for the network in Fig. 9.27.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

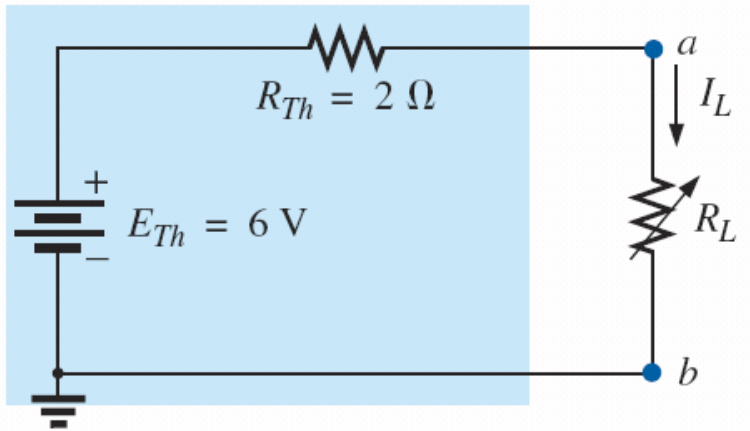


FIG. 9.31 Substituting the Thévenin equivalent circuit for the network external to  $R_L$  in Fig. 9.26.


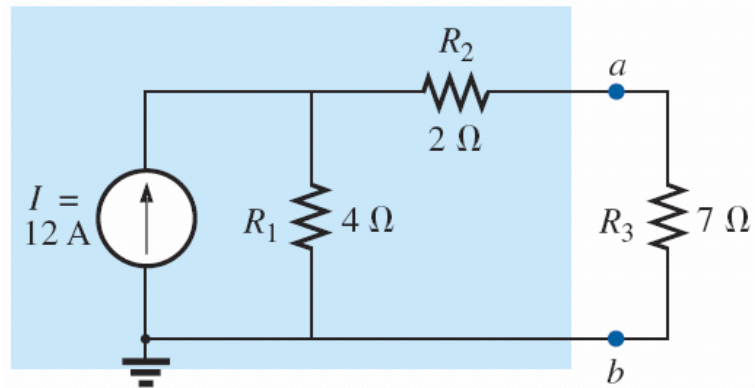


FIG. 9.32 Example 9.7.

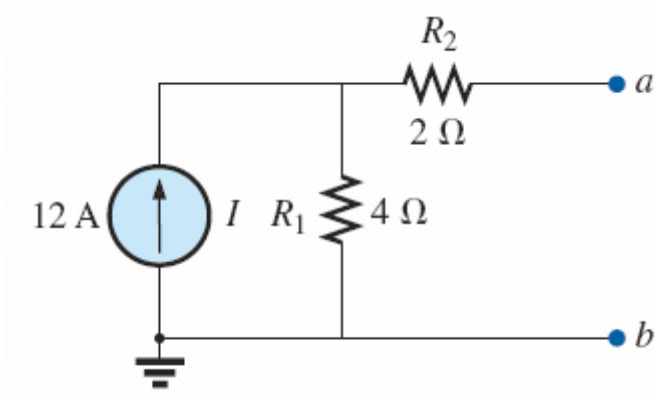


# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure



**FIG. 9.33** Establishing the terminals of particular interest for the network in Fig. 9.32.

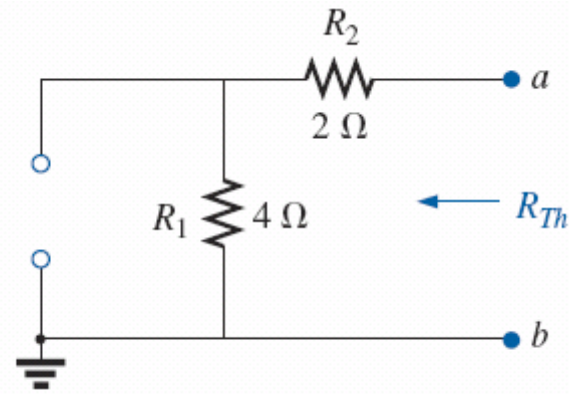

**FIG. 9.34** Determining  $R_{Th}$  for the network in Fig. 9.33.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

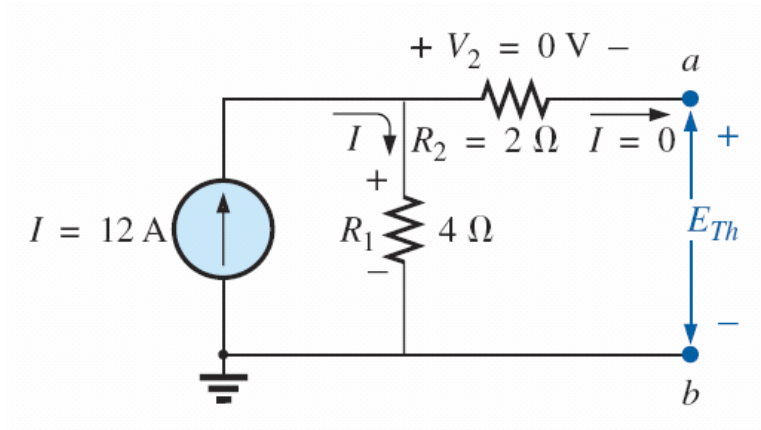


FIG. 9.35 Determining  $E_{Th}$  for the network in Fig. 9.33.

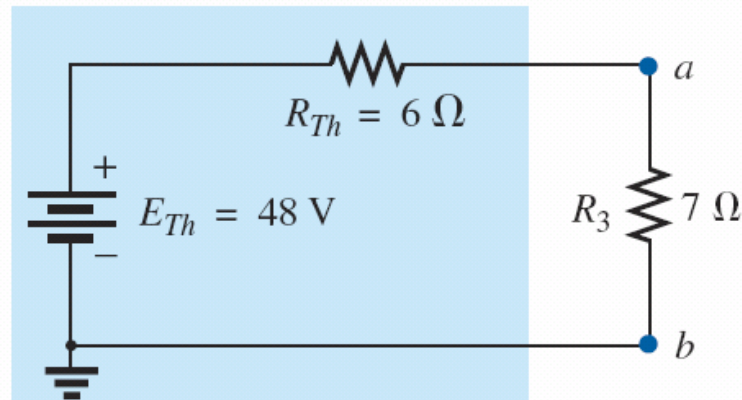


FIG. 9.36 Substituting the Thévenin equivalent circuit in the network external to the resistor  $R_3$  in Fig. 9.32.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure


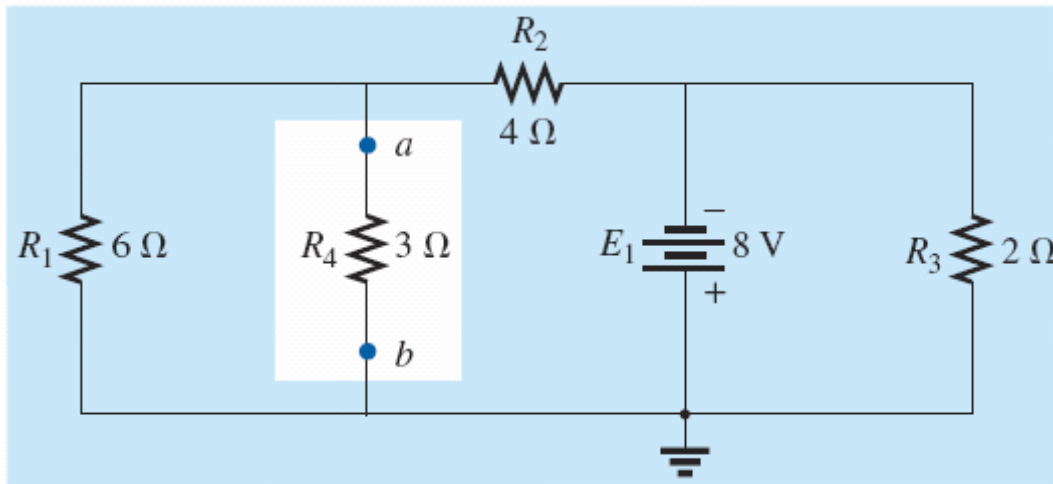


FIG. 9.37 Example 9.8.

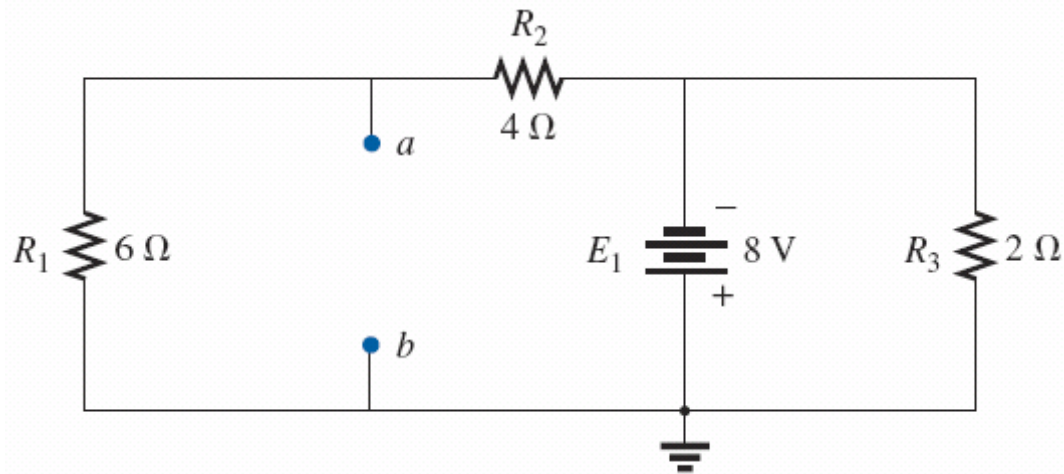

# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure



**FIG. 9.38** *Identifying the terminals of particular interest for the network in Fig. 9.37.*



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

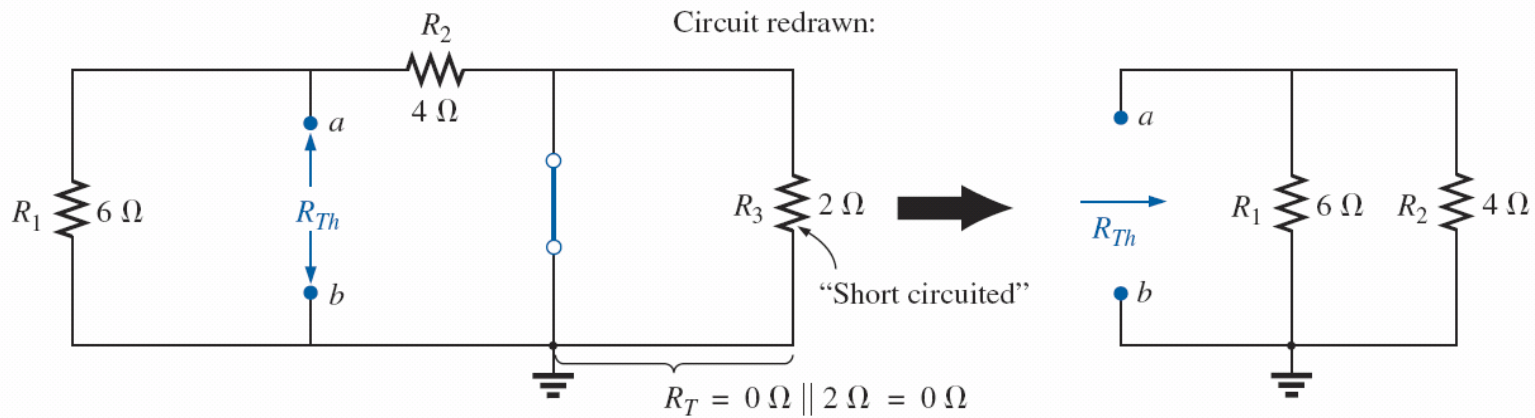


FIG. 9.39 Determining  $R_{Th}$  for the network in Fig. 9.38.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

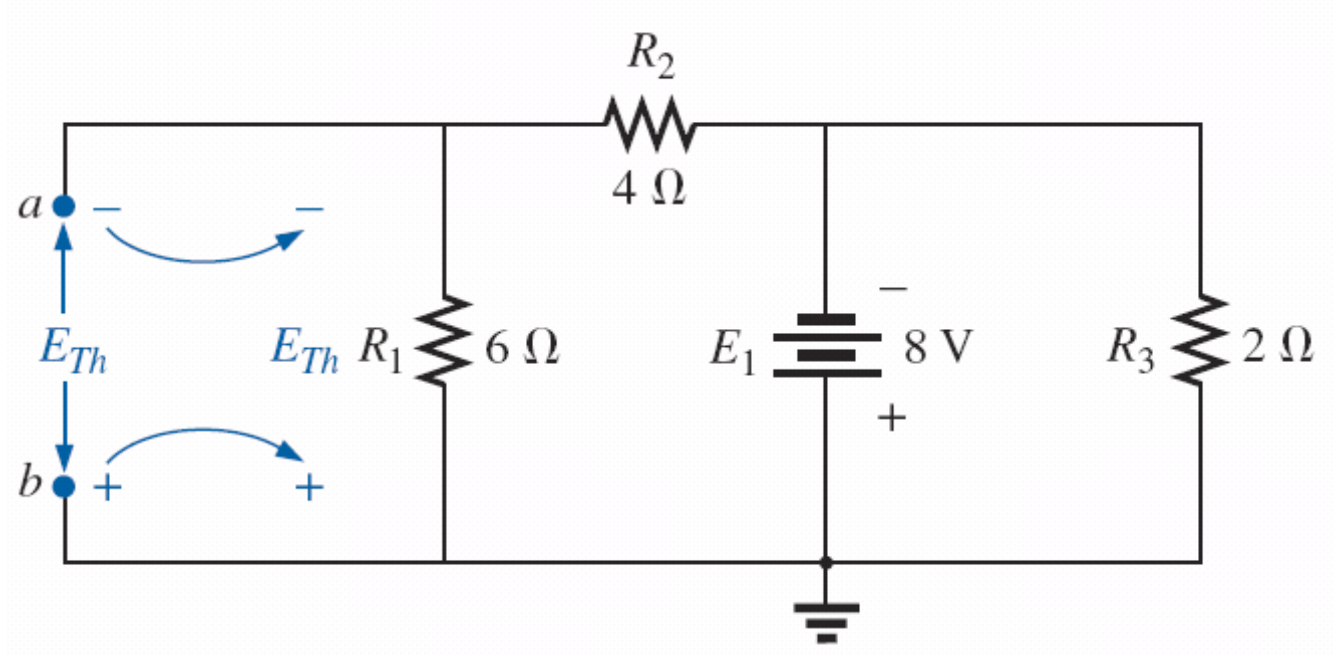


FIG. 9.40 Determining  $E_{Th}$  for the network in Fig. 9.38.





# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

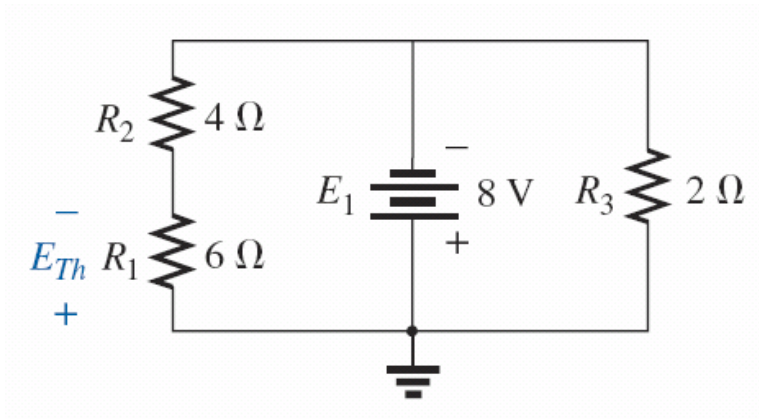


FIG. 9.41 Network of Fig. 9.40 redrawn.

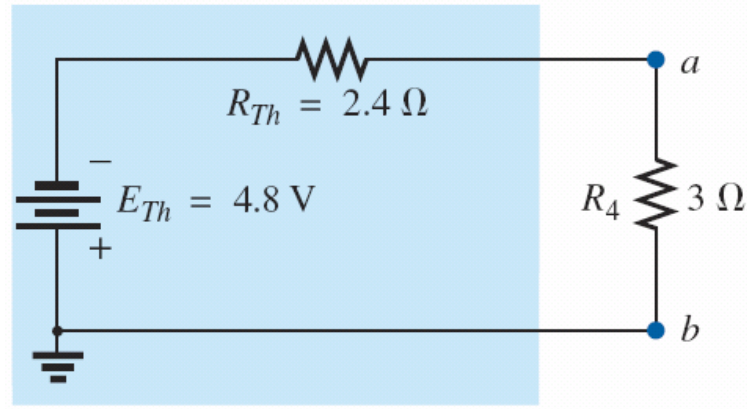


FIG. 9.42 Substituting the Thévenin equivalent circuit for the network external to the resistor  $R_4$  in Fig. 9.37.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure


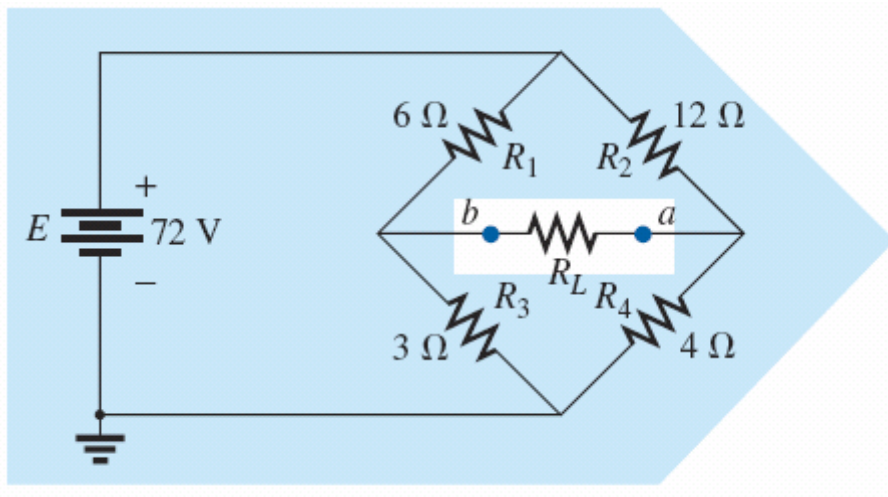


FIG. 9.43 Example 9.9.

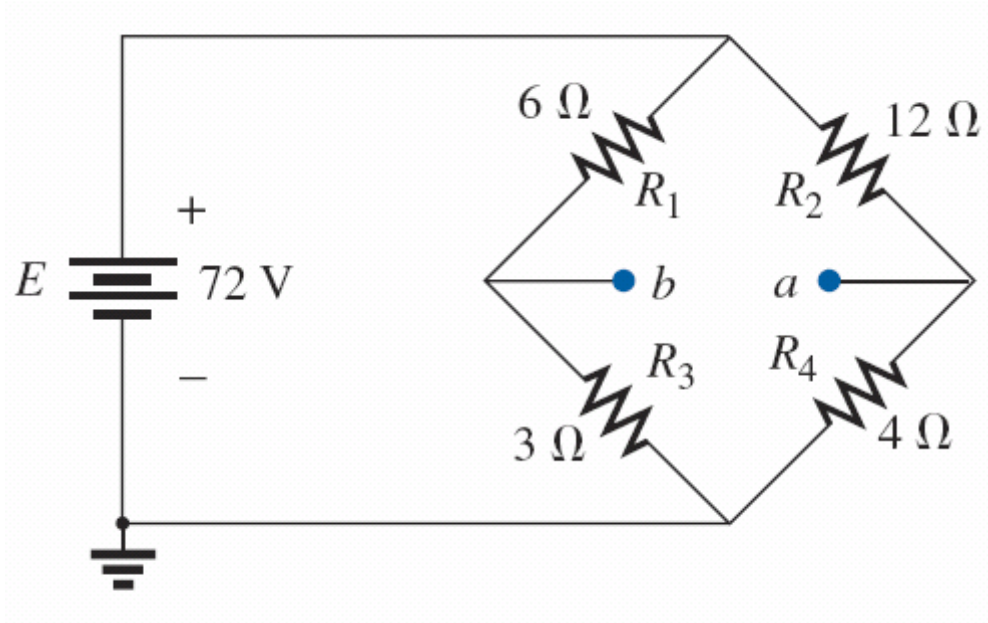

# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure



**FIG. 9.44** Identifying the terminals of particular interest for the network in Fig. 9.43.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

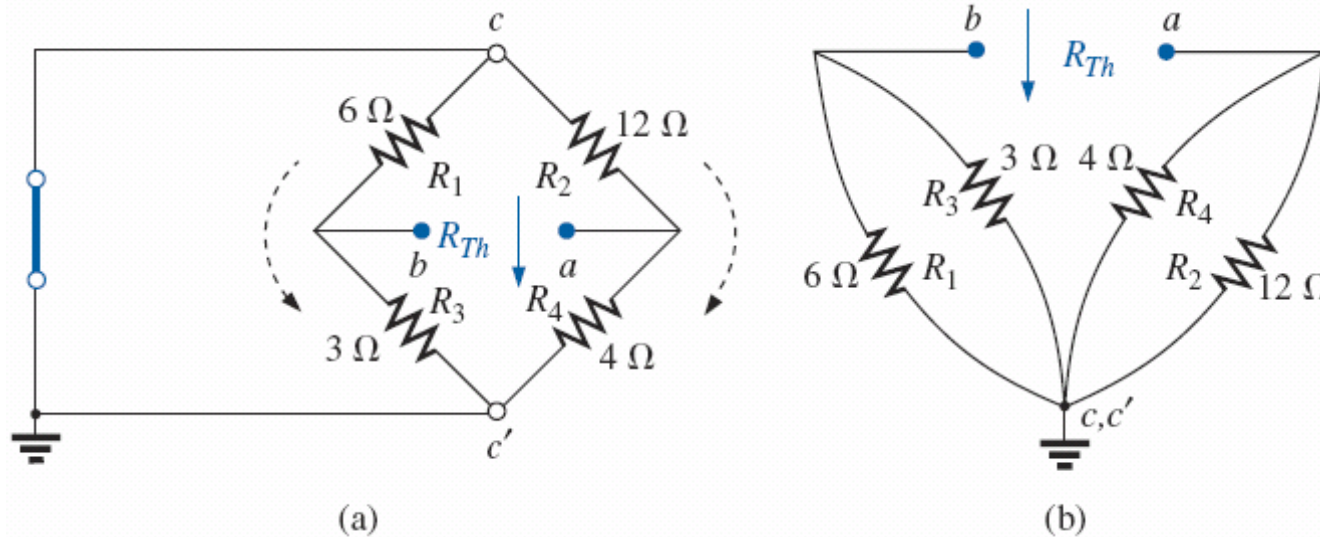


FIG. 9.45 Solving for  $R_{Th}$  for the network in Fig. 9.44.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure


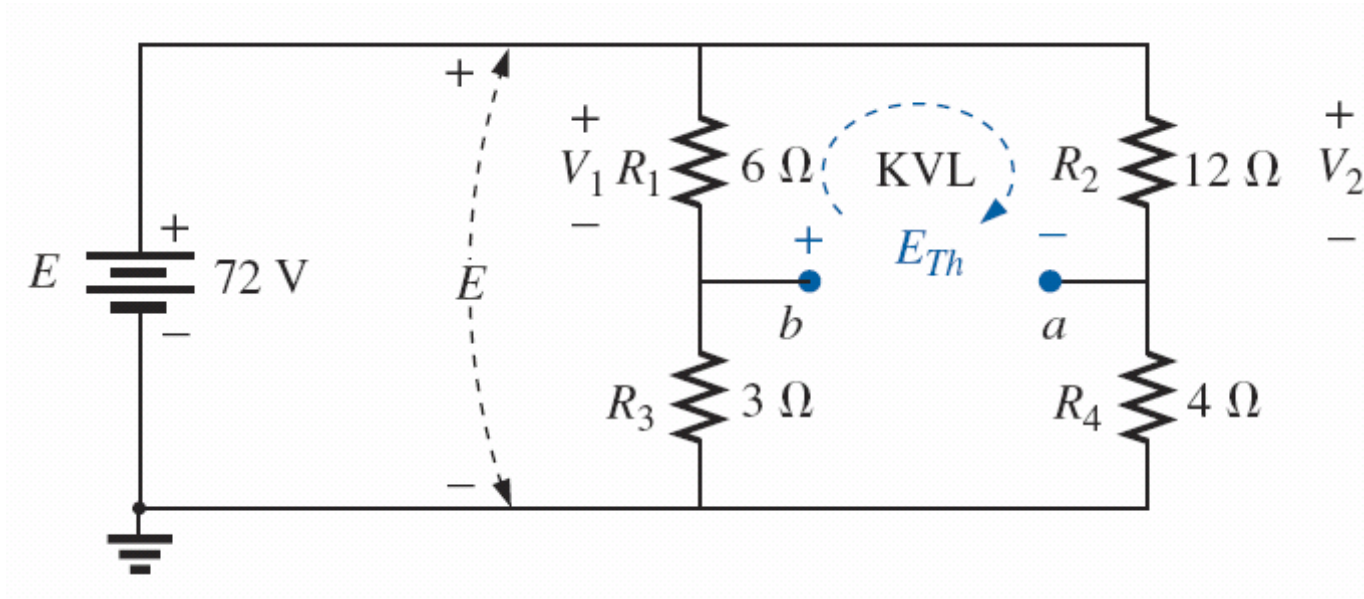


FIG. 9.46 Determining  $E_{Th}$  for the network in Fig. 9.44.

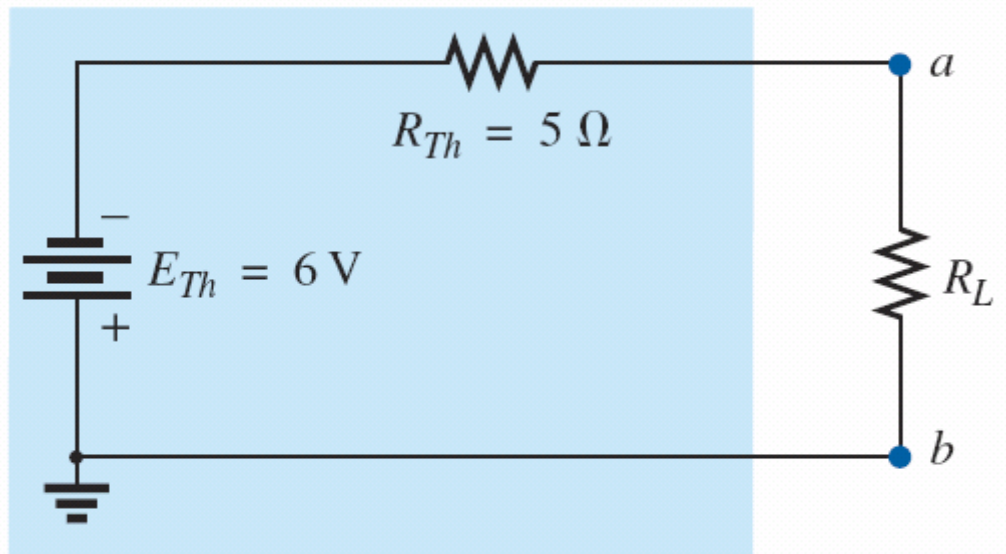

# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure



**FIG. 9.47** *Substituting the Thévenin equivalent circuit for the network external to the resistor  $R_L$  in Fig. 9.43.*



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure


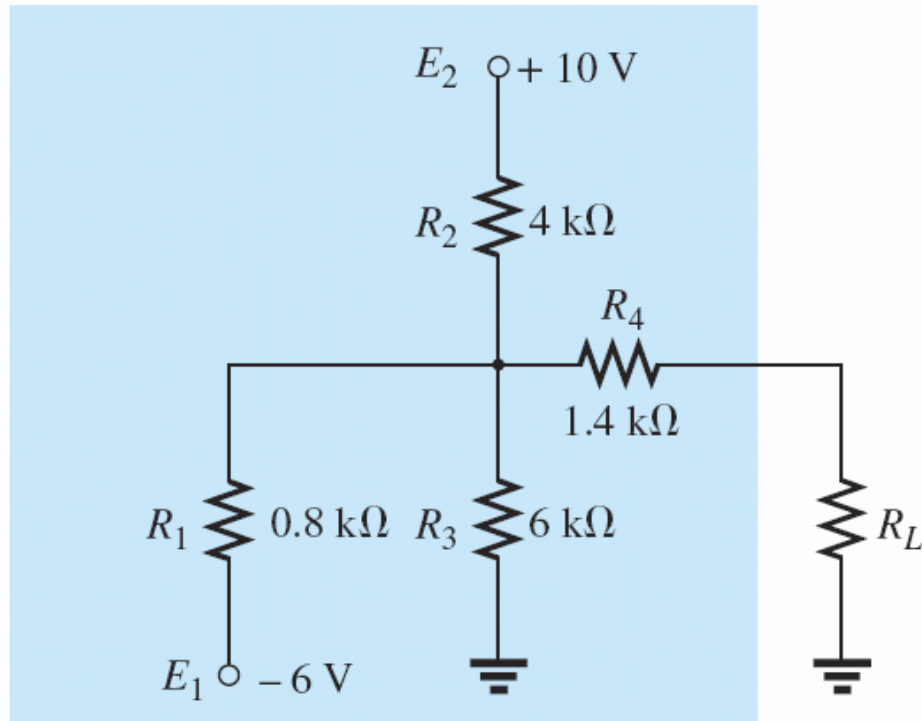


FIG. 9.48 Example 9.10.

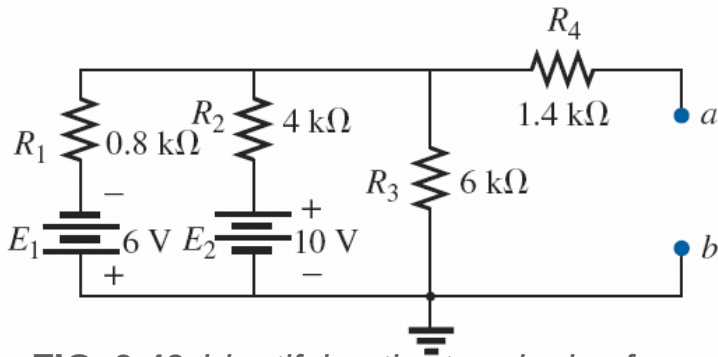


# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure



**FIG. 9.49** Identifying the terminals of particular interest for the network in Fig. 9.48.

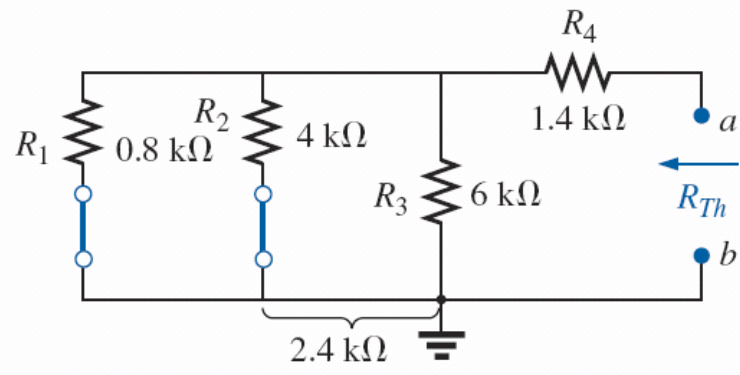


**FIG. 9.50** Determining  $R_{Th}$  for the network in Fig. 9.49.






# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

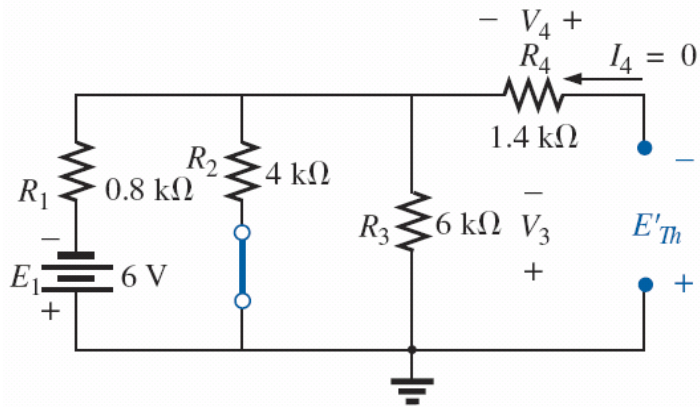

**FIG. 9.51** Determining the contribution to  $E_{Th}$  from the source  $E_1$  for the network in Fig. 9.49.

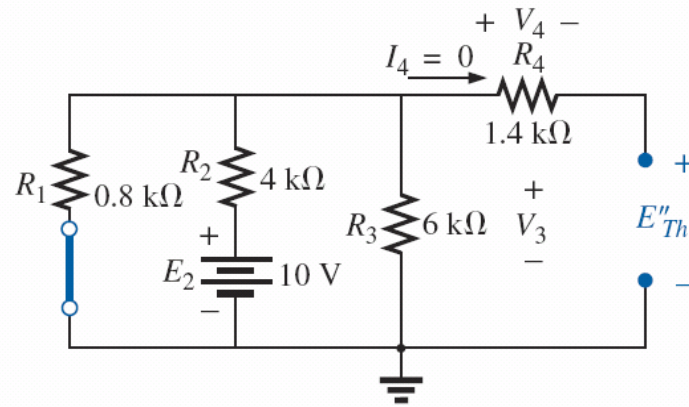


**FIG. 9.52** Determining the contribution to  $E_{Th}$  from the source  $E_2$  for the network in Fig. 9.49.



# THÉVENIN'S THEOREM

## Thévenin's Theorem Procedure

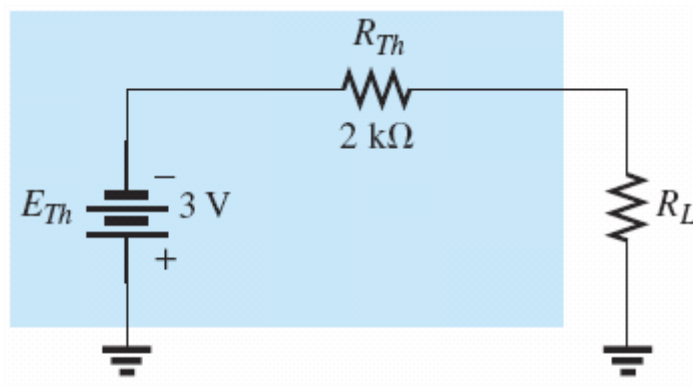

**FIG. 9.53** *Substituting the Thévenin equivalent circuit for the network external to the resistor  $R_L$  in Fig. 9.48.*



# THÉVENIN'S THEOREM

## Experimental Procedures

❖ Measuring  $E_{th}$


❖ Measuring  $R_{Th}$





# THÉVENIN'S THEOREM

## Experimental Procedures

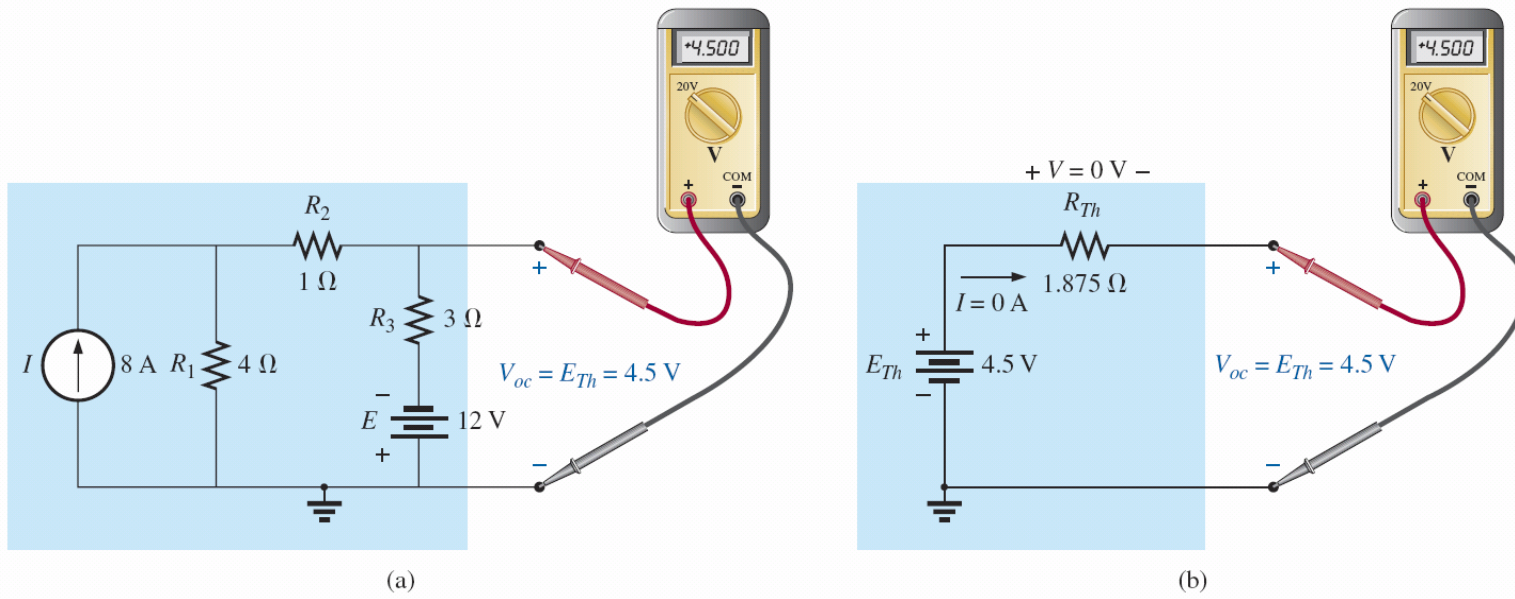

**FIG. 9.54** Measuring the Thévenin voltage with a voltmeter: (a) actual network; (b) Thévenin equivalent.



# THÉVENIN'S THEOREM

## Experimental Procedures


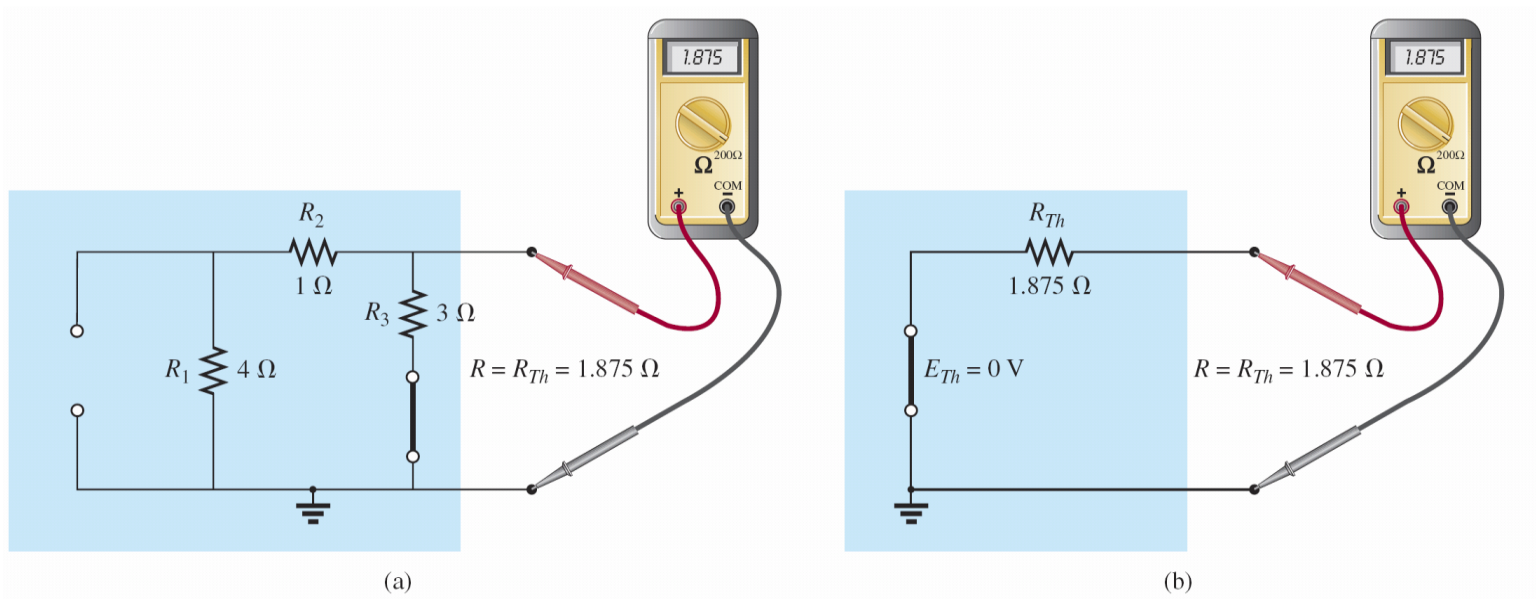


FIG. 9.55 Measuring  $R_{Th}$  with an ohmmeter: (a) actual network; (b) Thévenin equivalent.

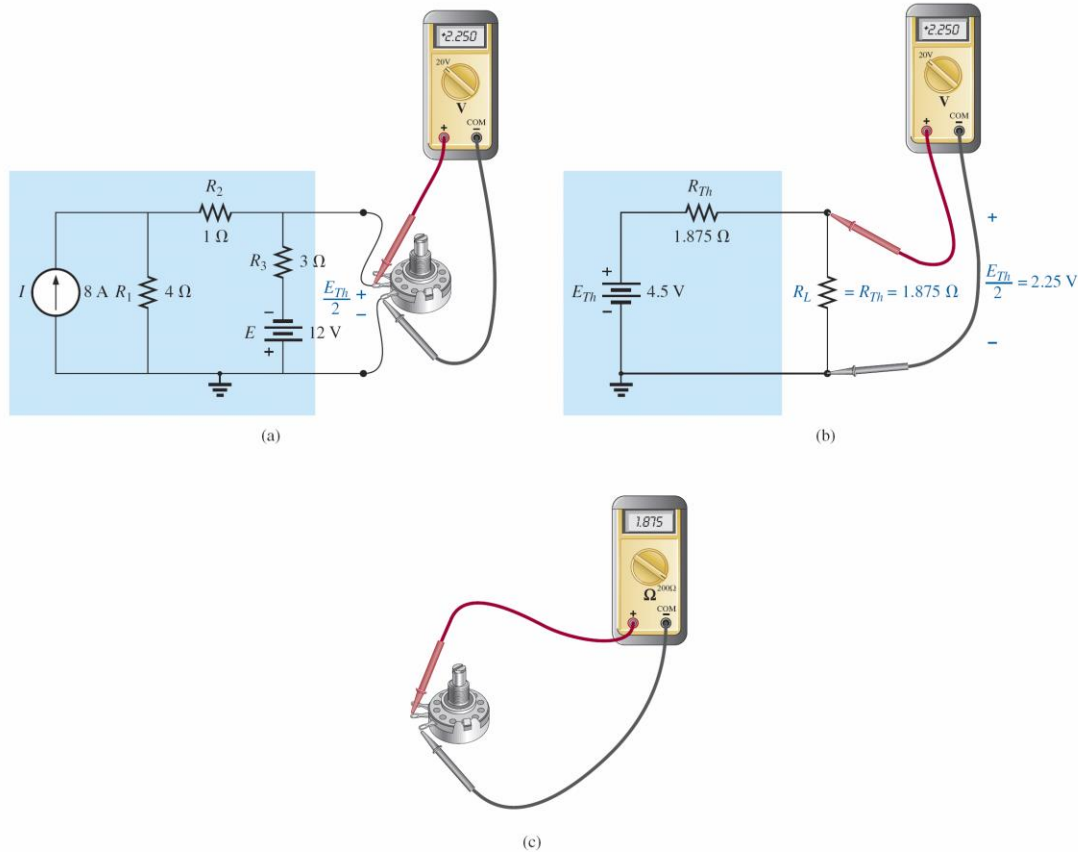

# THÉVENIN'S THEOREM

## Experimental Procedures

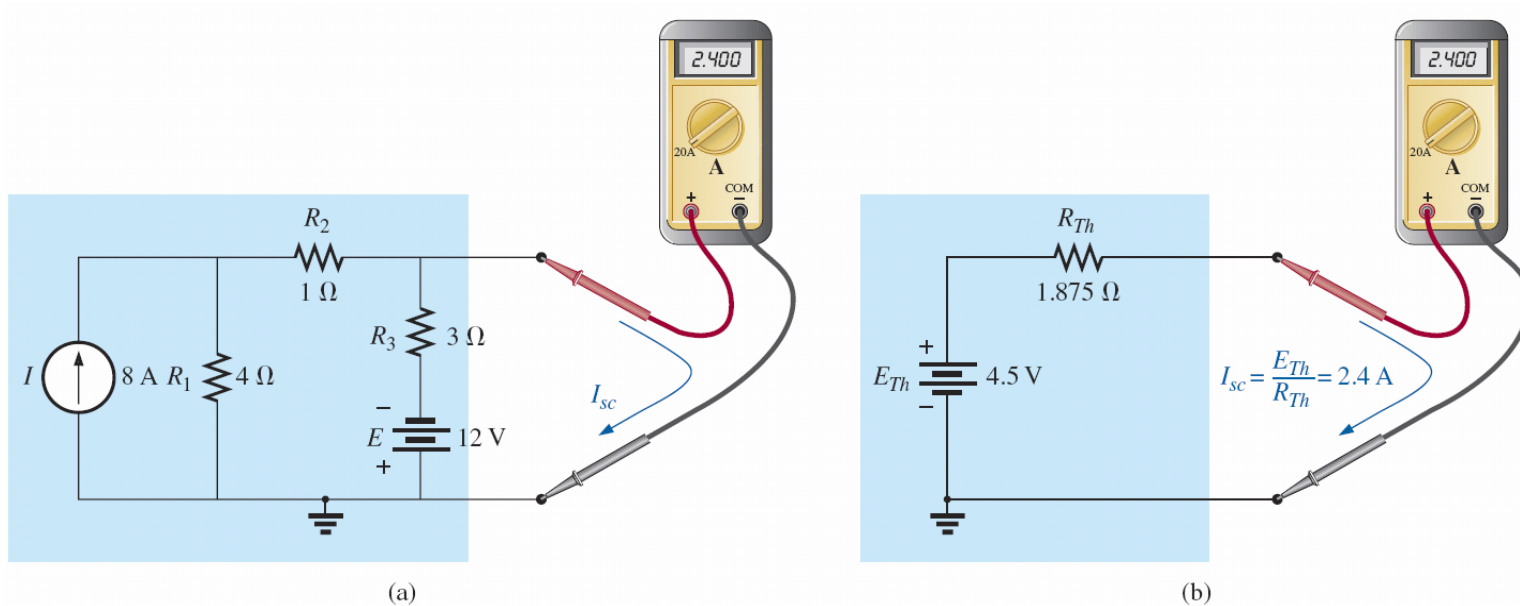


**FIG. 9.56** Using a potentiometer to determine  $R_{Th}$ : (a) actual network; (b) Thévenin equivalent; (c) measuring  $R_{Th}$ .



# THÉVENIN'S THEOREM

## Experimental Procedures



**FIG. 9.57** Determining  $R_{Th}$  using the short-circuit current: (a) actual network; (b) Thévenin equivalent.



# NORTON'S THEOREM

- ❖ In Section 8.3, we learned that every voltage source with a series internal resistance has a current source equivalent.
- ❖ The current source equivalent can be determined by **Norton's theorem**. It can also be found through the conversions of Section 8.3.
- ❖ The theorem states the following:
  - *Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor, as shown in Fig. 9.59*







# NORTON'S THEOREM

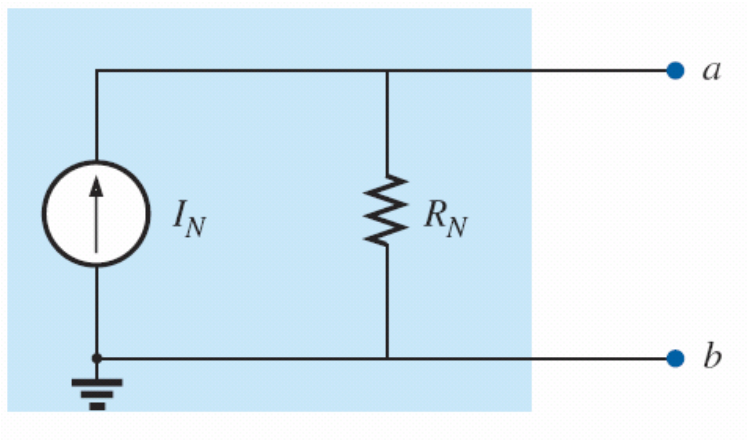


FIG. 9.59 Norton equivalent circuit.



# NORTON'S THEOREM

## Norton's Theorem Procedure

### ❖ *Preliminary:*

- *1. Remove that portion of the network across which the Norton equivalent circuit is found.*
- *2. Mark the terminals of the remaining two-terminal network.*





# NORTON'S THEOREM

## Norton's Theorem Procedure

❖  $R_N$ :



- *3. Calculate  $R_N$  by first setting all sources to zero (voltage sources are replaced with short circuits and current sources with open circuits) and then finding the resultant resistance between the two marked terminals. (If the internal resistance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.) Since  $R_N = R_{Th}$ , the procedure and value obtained using the approach described for Thévenin's theorem will determine the proper value of  $R_N$ .*



# NORTON'S THEOREM

## Norton's Theorem Procedure

❖  $I_N$ :



- 4. Calculate  $I_N$  by first returning all sources to their original position and then finding the short-circuit current between the marked terminals. It is the same current that would be measured by an ammeter placed between the marked terminals.



# NORTON'S THEOREM

## Norton's Theorem Procedure

### ❖ *Conclusion:*

- *5. Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.*





# NORTON'S THEOREM

## Norton's Theorem Procedure

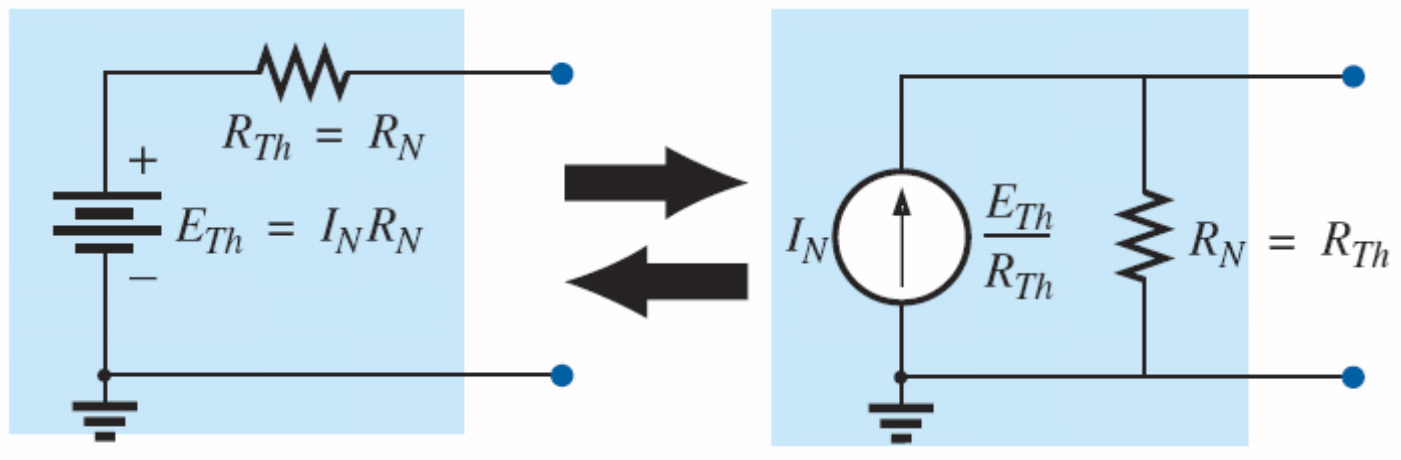


FIG. 9.60 Converting between Thévenin and Norton equivalent circuits.



# NORTON'S THEOREM

## Norton's Theorem Procedure

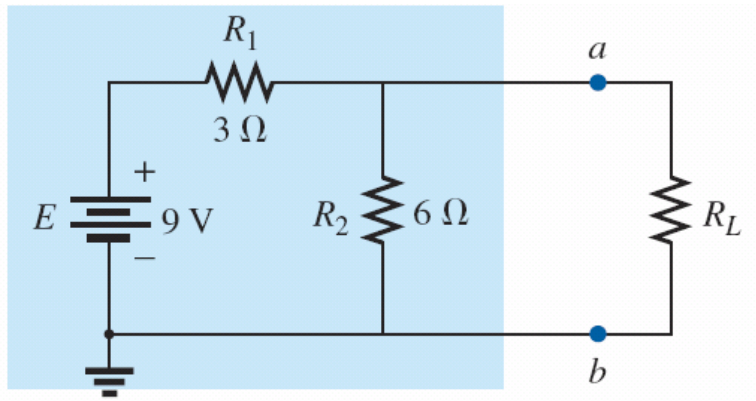


FIG. 9.61 Example 9.11.


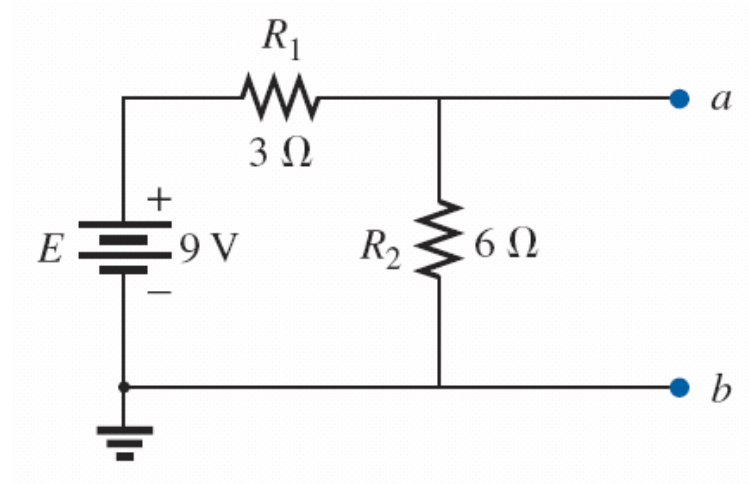


FIG. 9.62 Identifying the terminals of particular interest for the network in Fig. 9.61.

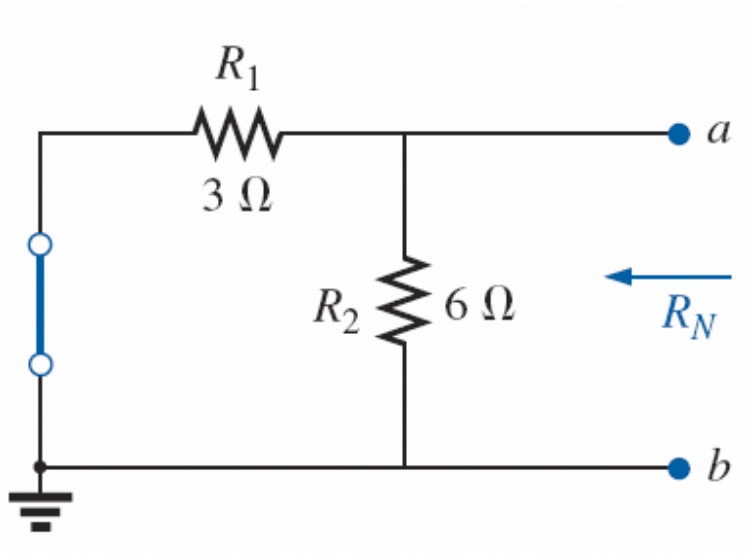


# NORTON'S THEOREM

## Norton's Theorem Procedure



**FIG. 9.63** Determining  $R_N$  for the network in Fig. 9.62.

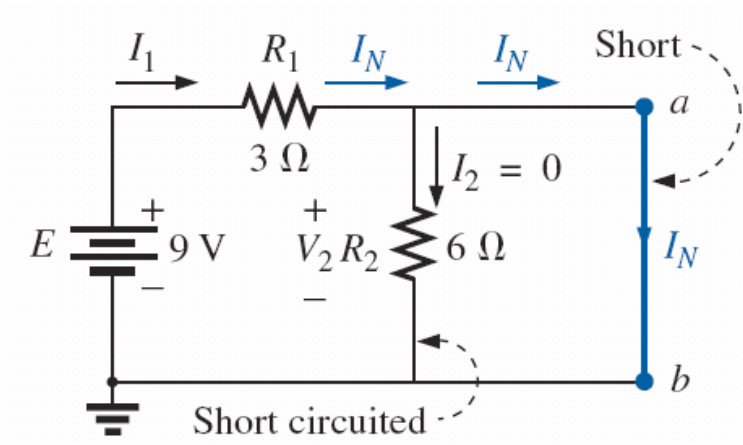


**FIG. 9.64** Determining  $I_N$  for the network in Fig. 9.62.





# NORTON'S THEOREM

## Norton's Theorem Procedure

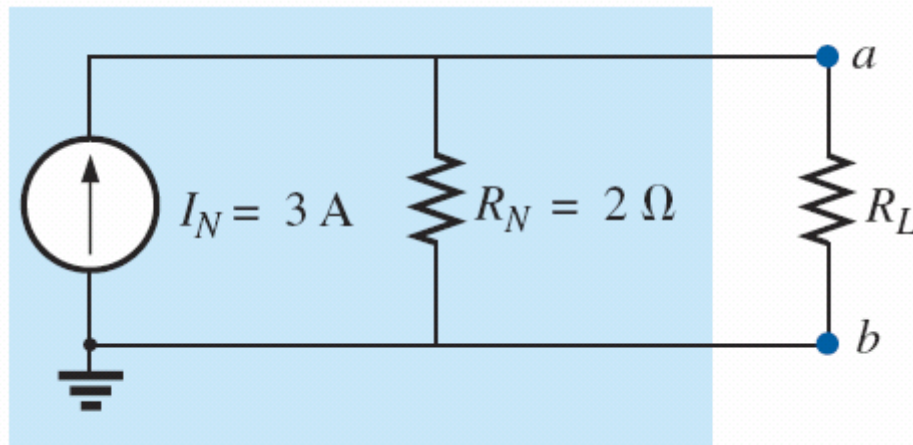


**FIG. 9.65** *Substituting the Norton equivalent circuit for the network external to the resistor  $R_L$  in Fig. 9.61.*



# NORTON'S THEOREM

## Norton's Theorem Procedure

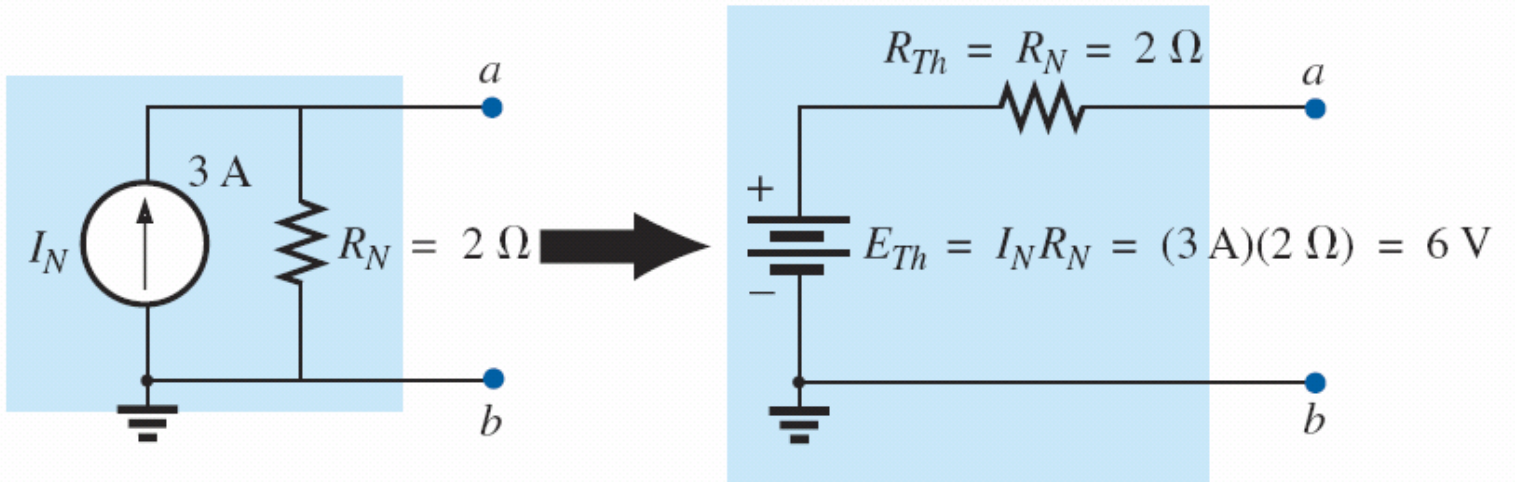

**FIG. 9.66** Converting the Norton equivalent circuit in Fig. 9.65 to a Thévenin equivalent circuit.



# NORTON'S THEOREM

## Norton's Theorem Procedure

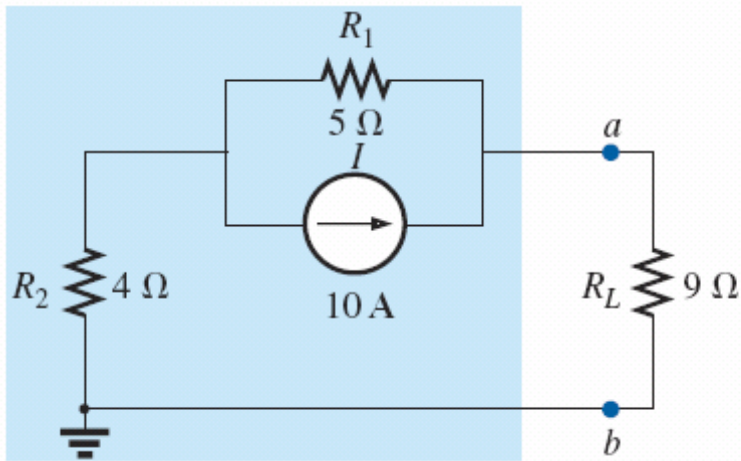


FIG. 9.67 Example 9.12.


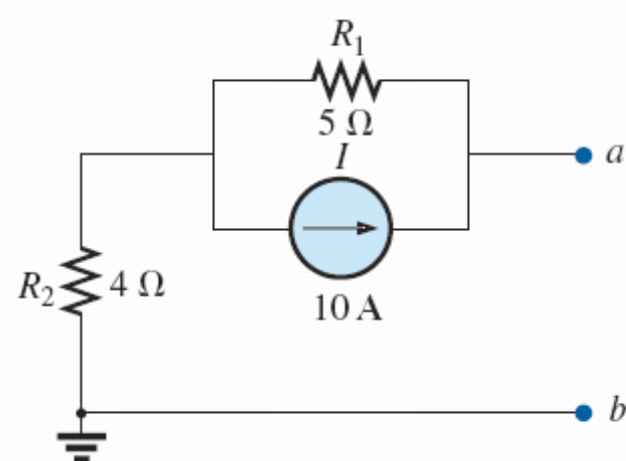


FIG. 9.68 Identifying the terminals of particular interest for the network in Fig. 9.67.

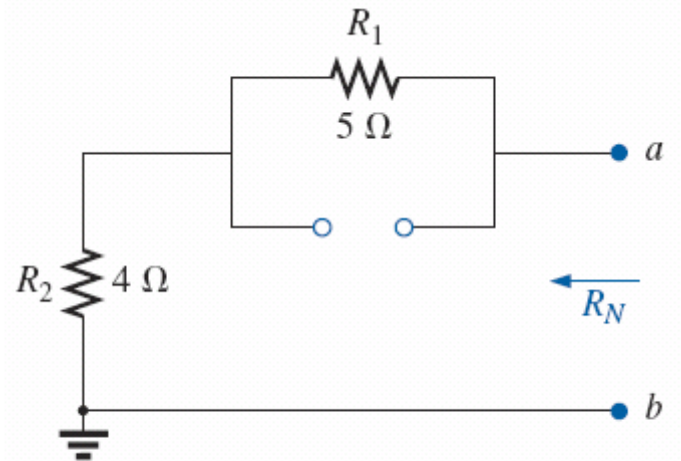

# NORTON'S THEOREM

## Norton's Theorem Procedure



**FIG. 9.69** Determining  $R_N$  for the network in Fig. 9.68.



# NORTON'S THEOREM

## Norton's Theorem Procedure


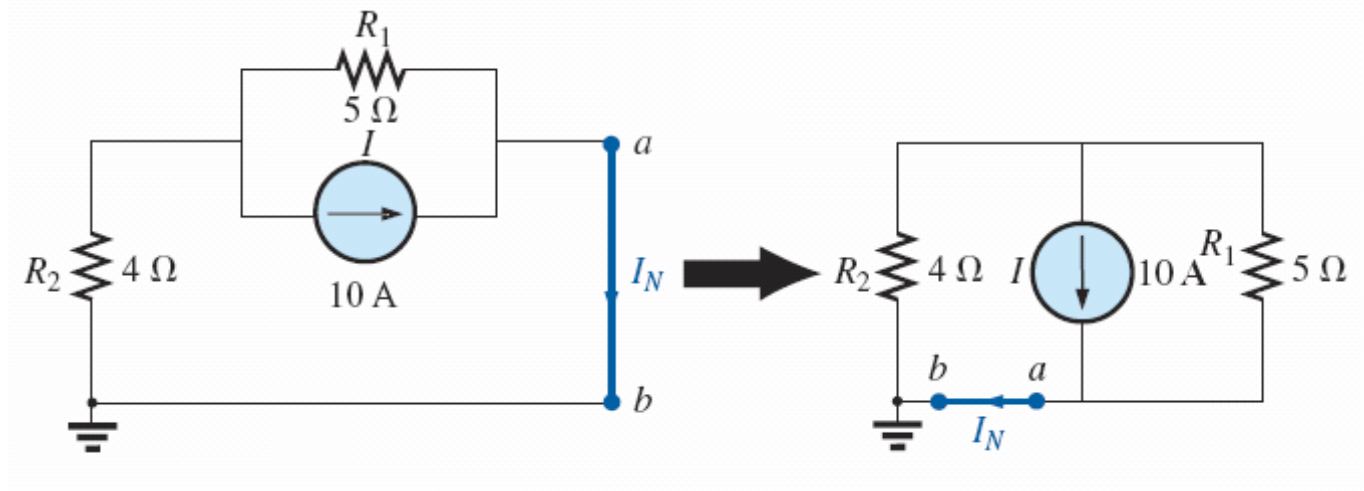


FIG. 9.70 Determining  $I_N$  for the network in Fig. 9.68.

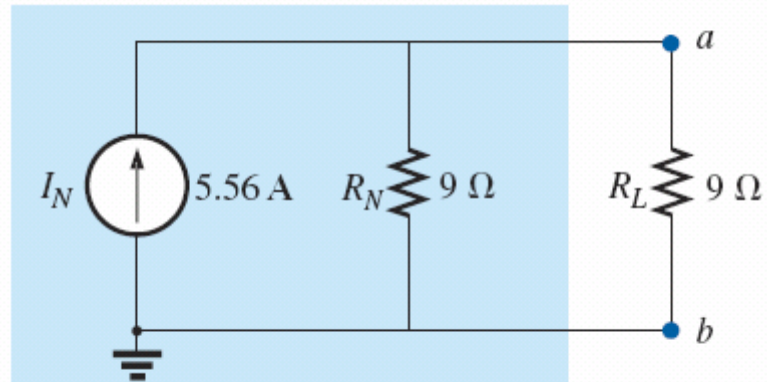

# NORTON'S THEOREM

## Norton's Theorem Procedure



**FIG. 9.71** *Substituting the Norton equivalent circuit for the network external to the resistor  $R_L$  in Fig. 9.67.*





# NORTON'S THEOREM

## Norton's Theorem Procedure


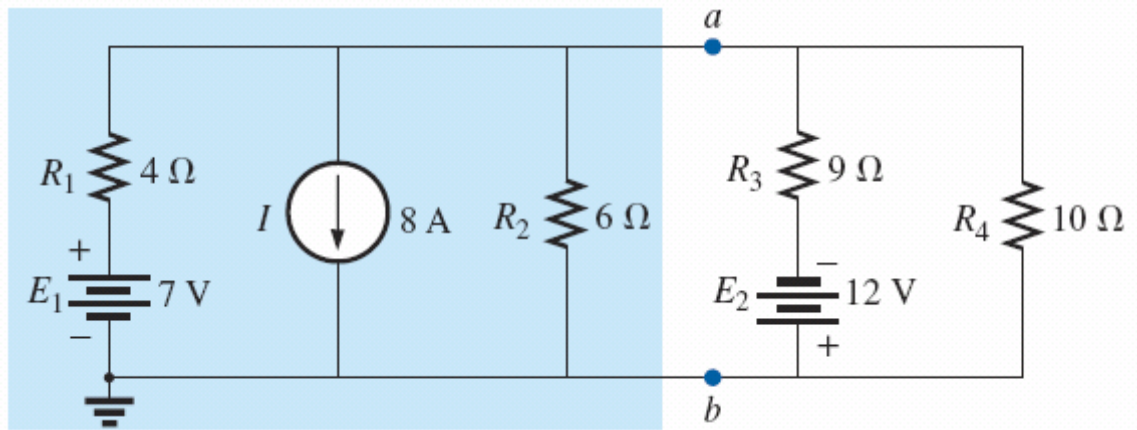


FIG. 9.72 Example 9.13.

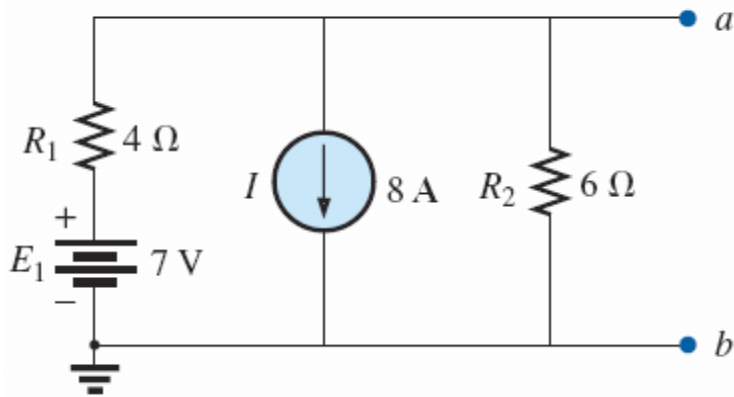


# NORTON'S THEOREM

## Norton's Theorem Procedure



**FIG. 9.73** Identifying the terminals of particular interest for the network in Fig. 9.72.

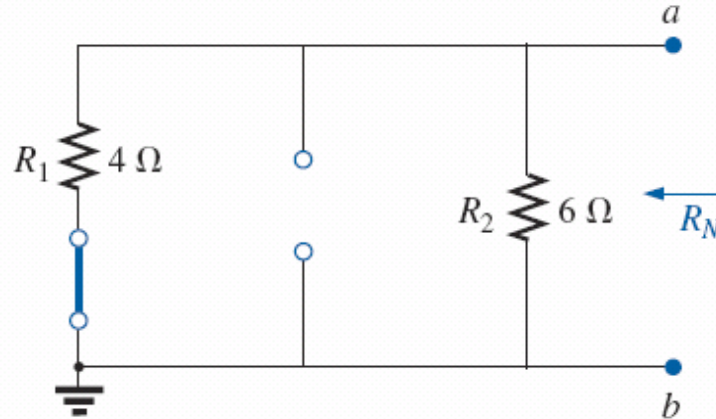

**FIG. 9.74** Determining  $R_N$  for the network in Fig. 9.73.





# NORTON'S THEOREM

## Norton's Theorem Procedure

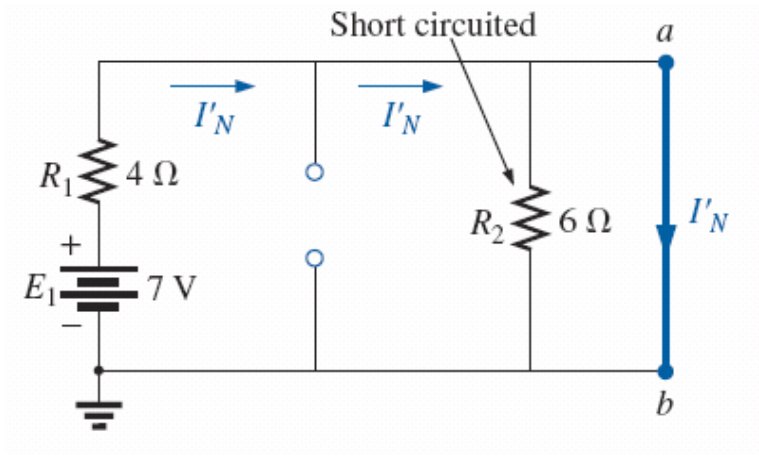


FIG. 9.75 Determining the contribution to  $I_N$  from the voltage source  $E_1$ .


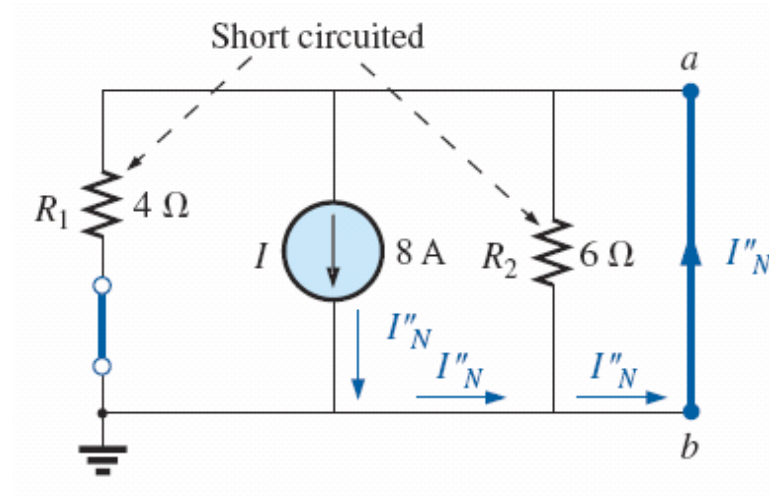


FIG. 9.76 Determining the contribution to  $I_N$  from the current source  $I$ .

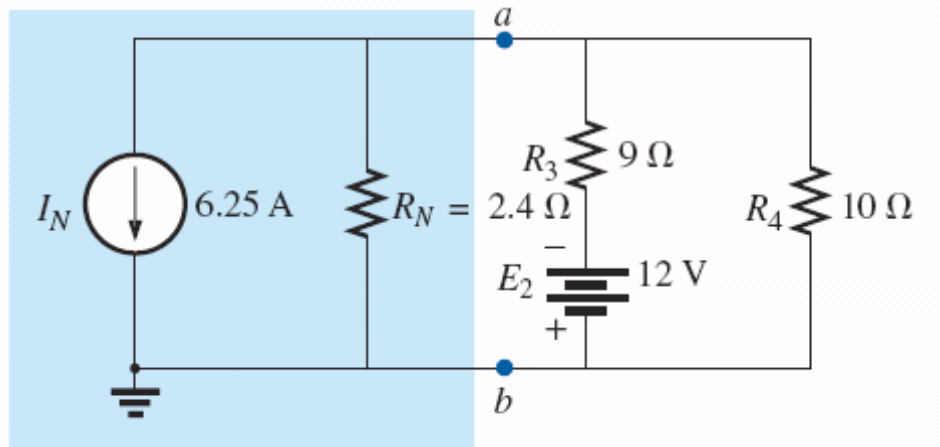

# NORTON'S THEOREM

## Norton's Theorem Procedure



**FIG. 9.77** Substituting the Norton equivalent circuit for the network to the left of terminals  $a$ - $b$  in Fig. 9.72.





# NORTON'S THEOREM

## Experimental Procedure

- ❖ The Norton current is measured in the same way as described for the short-circuit current ( $I_{sc}$ ) for the Thévenin network.
- ❖ Since the Norton and Thévenin resistances are the same, the same procedures can be followed as described for the Thévenin network.



# Thank You !

